


ELECTRONIC



DREAM BIG
AIM HIGH
NEVER GIVE UP

alinainanarif

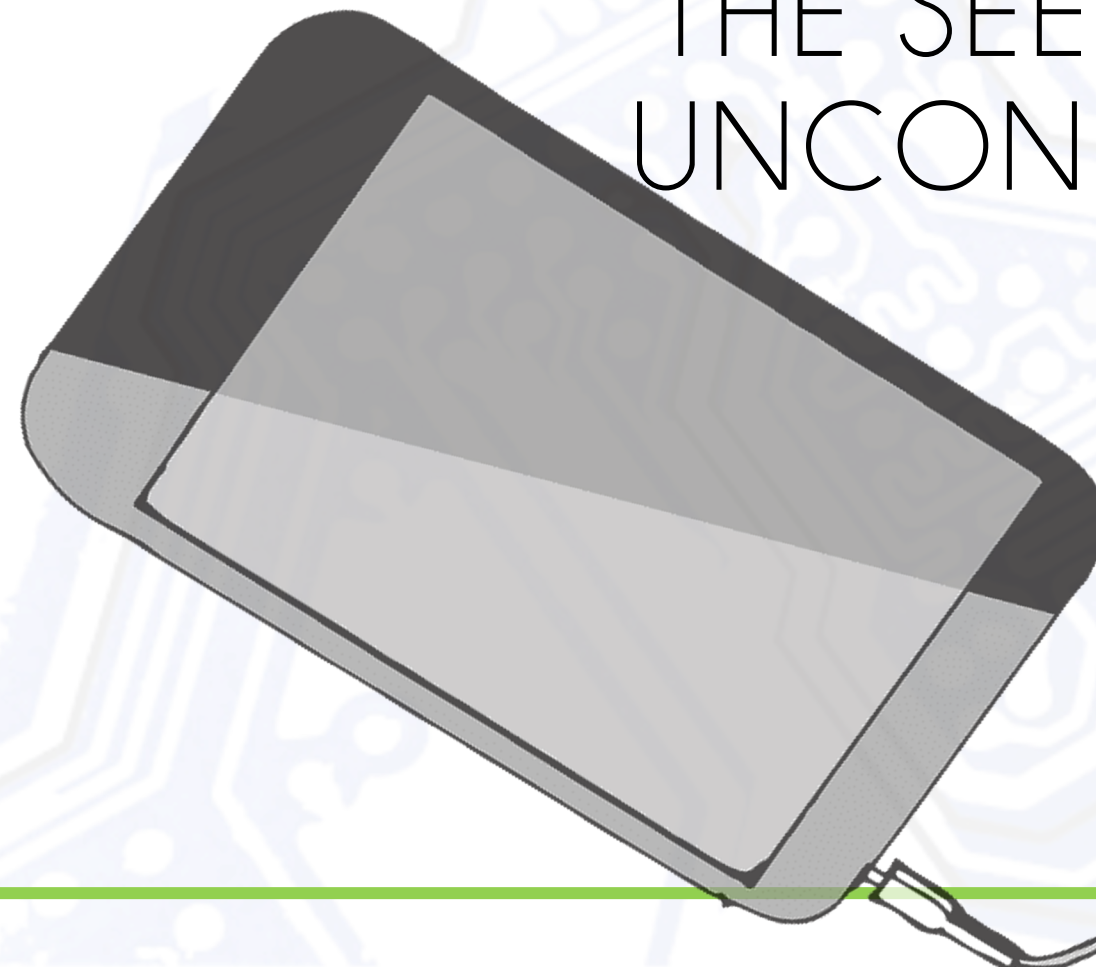
CREATIVITY
IS THE P^WWER
TO CONNECT
THE SEEMINGLY
UNCONNECTED






Thermionic emission

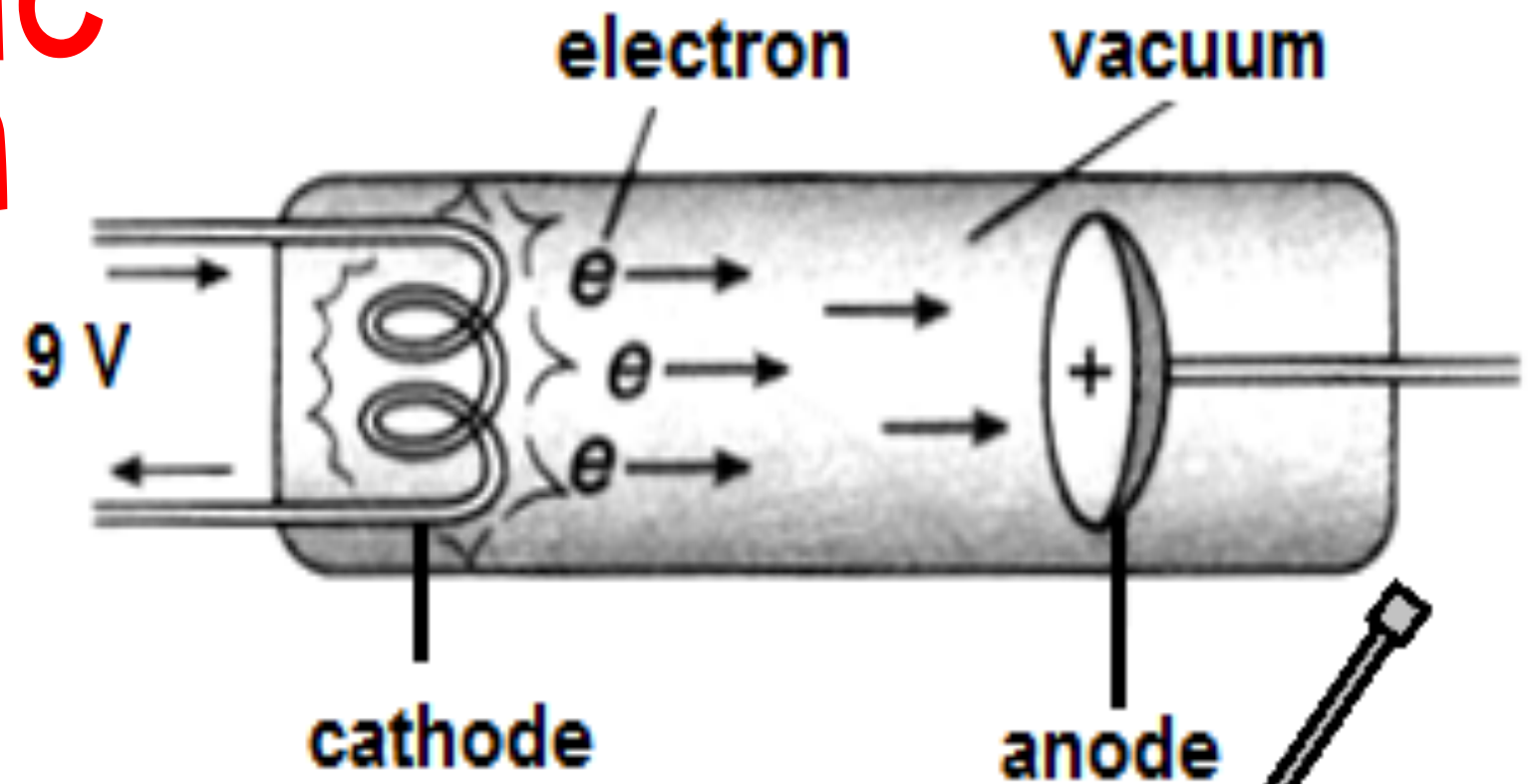is the process of emission of electrons from a heated metal's surface.




"To the electron -- may it never be of any use to anybody." -- JJ. Thomson's

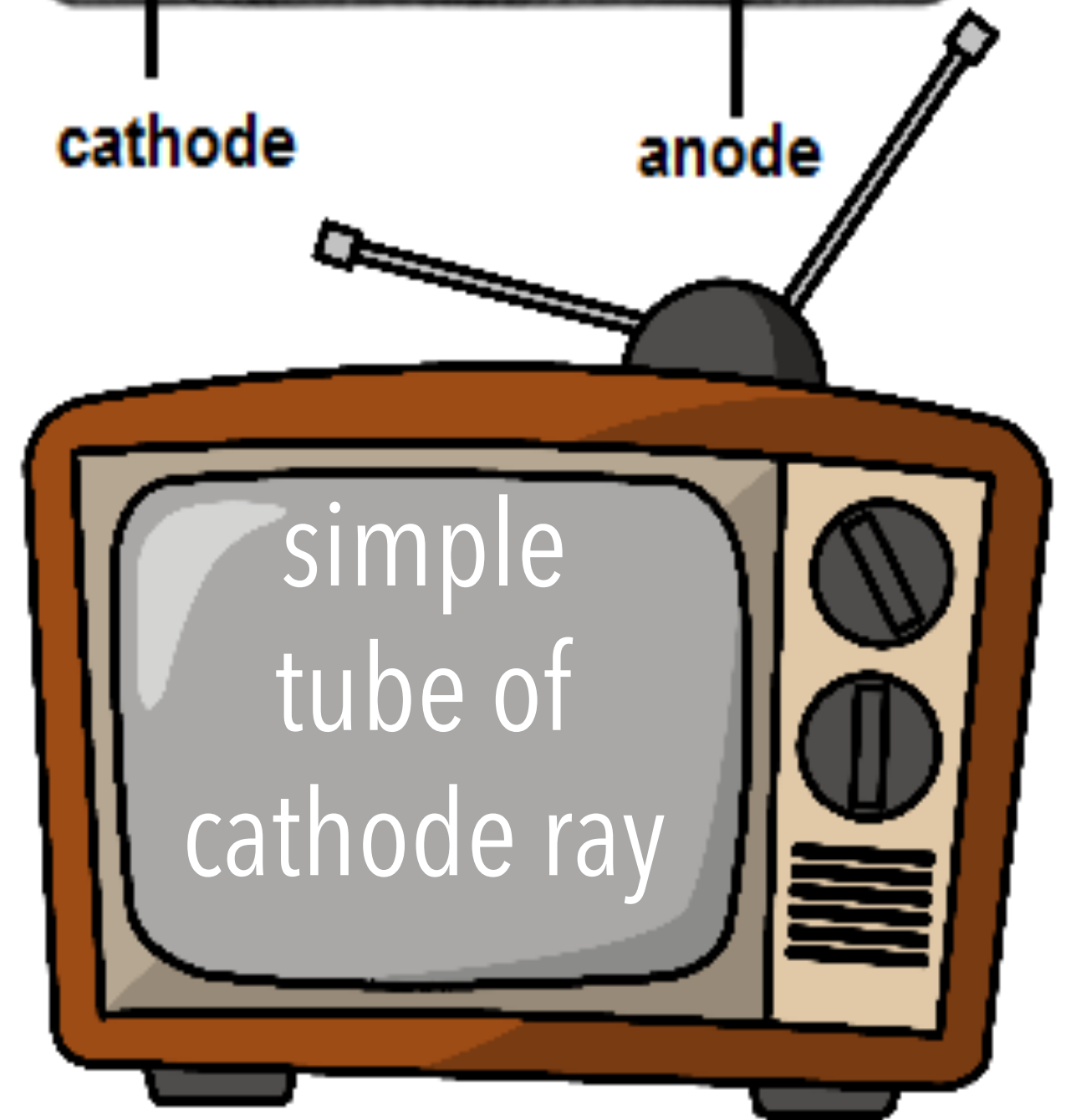Cathode ray A beam of electrons moving at high speed in a vacuum.




The properties of **Cathode rays**:

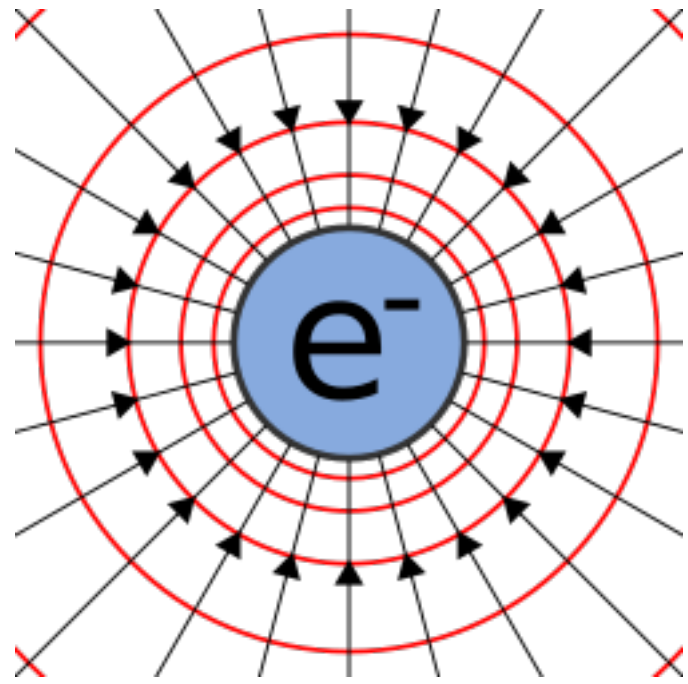


Negatively charged particles (electron)

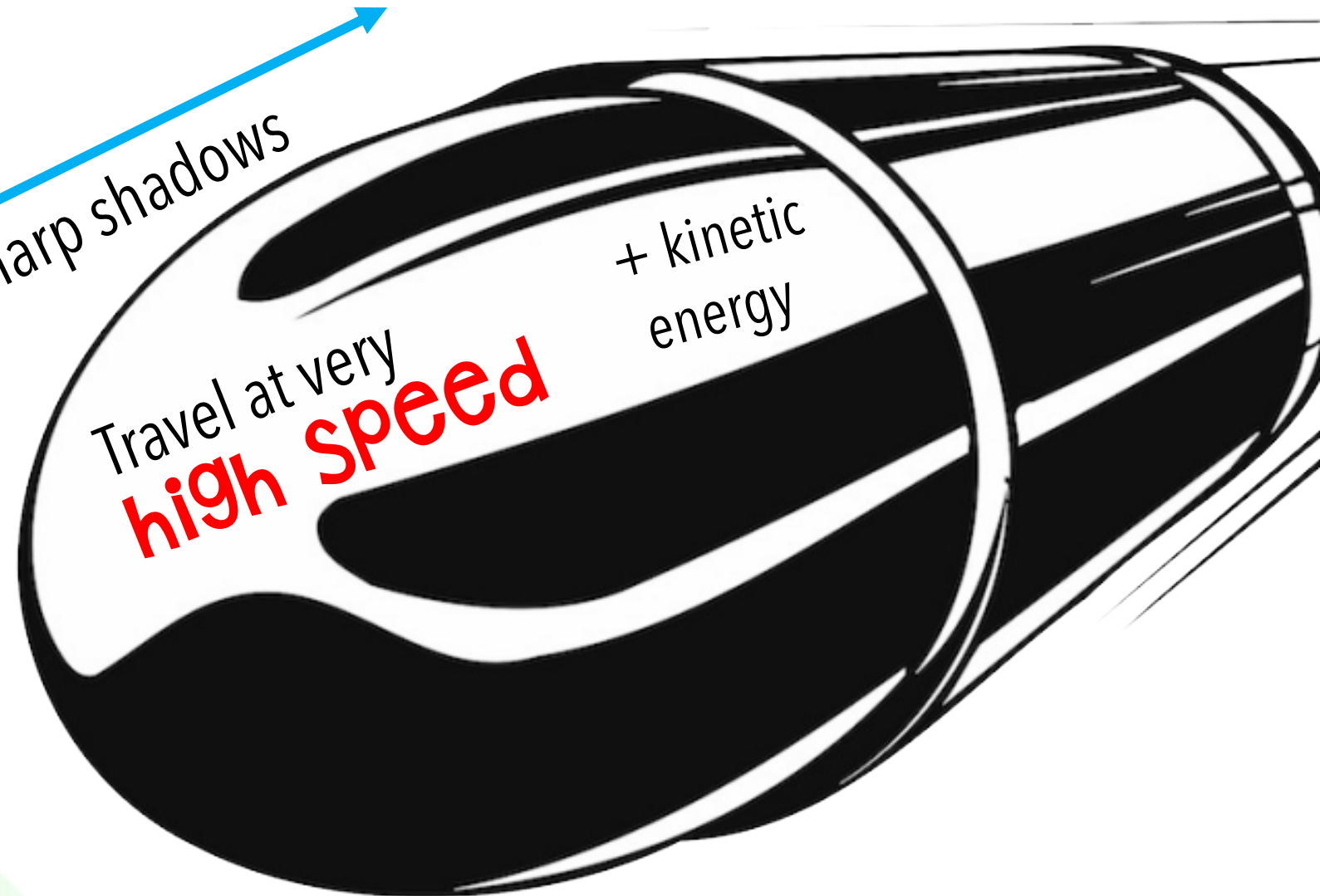Travel in **straight lines** and cast sharp shadows




Travel at very **high speed**

+ kinetic energy

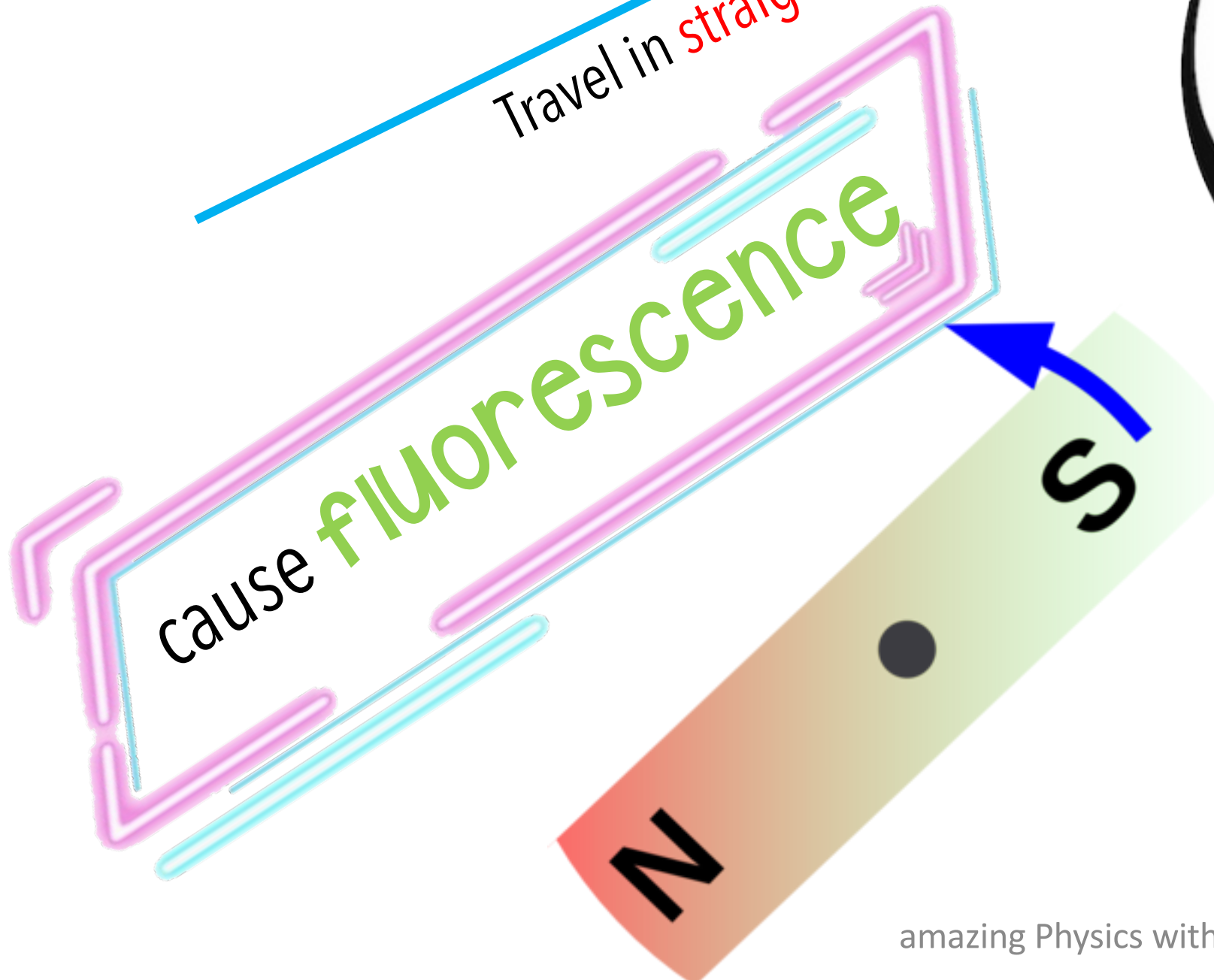

cause **fluorescence**

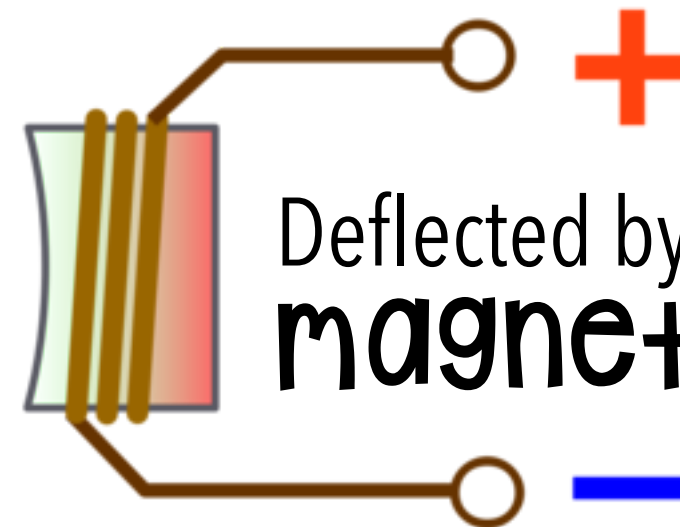

Deflected by **electric** and **magnetic fields**

Factors that influence the rate of thermionic emission:

FACTOR

EFFECT ON THE RATE OF THERMIONIC EMISSION

Temperature of the cathode

When the temperature of the cathode increases, the rate of thermionic emission increases.


Surface area of the cathode

A larger surface area of the cathode increases the rate of thermionic emission.

Potential difference between the anode and cathode.

The rate of thermionic emission is unchanged, when the potential difference increases, but the emitted electrons accelerate faster towards the anode.

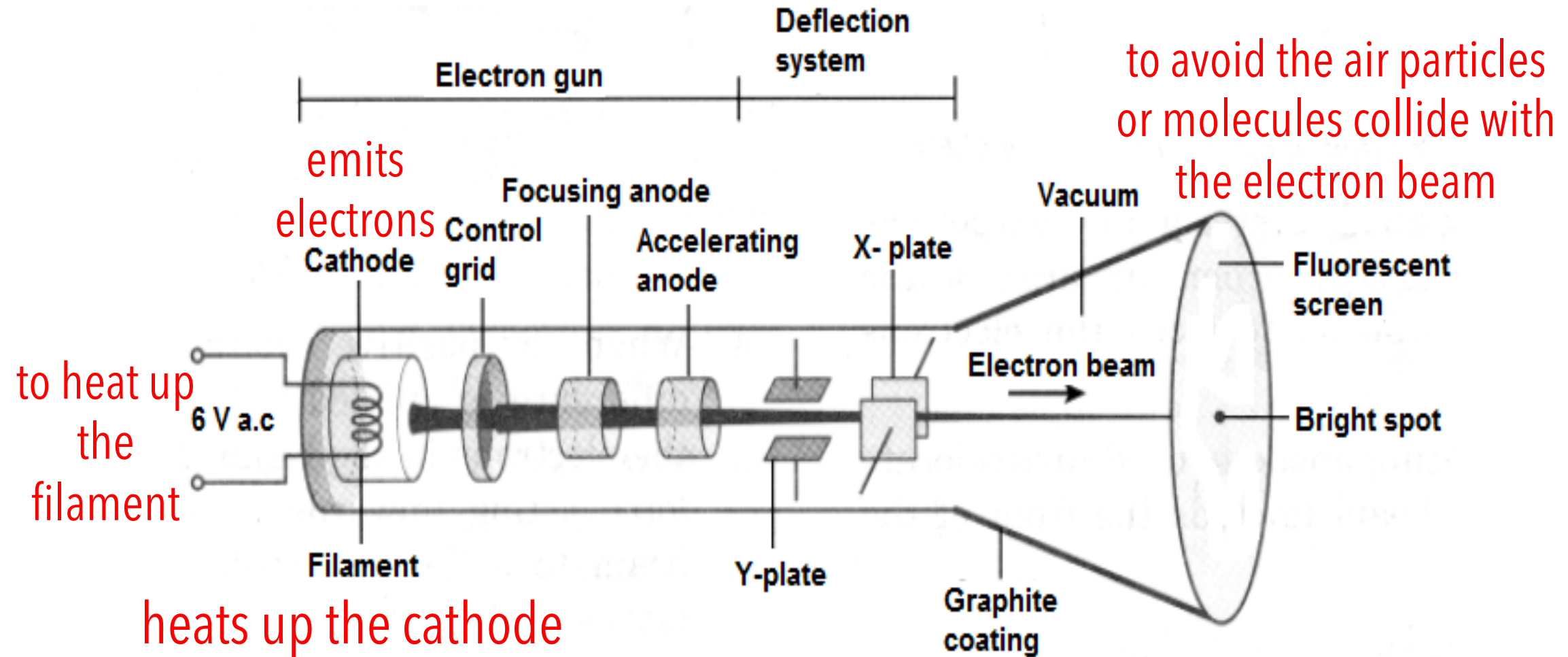STRUCTURE OF THE CATHODE RAY OSCILLOSCOPE



Transmission of energy in cathode ray:

Electrical energy → Kinetic energy + light energy + heat energy

$$\frac{1}{2}mv^2 = eV$$


$$v = \sqrt{\frac{2eV}{m}}$$

v = velocity of electron

V = Potential difference between Anode and Cathode (EHT)

e = Charge on 1 electron = $1.6 \times 10^{-19} \text{ C}$

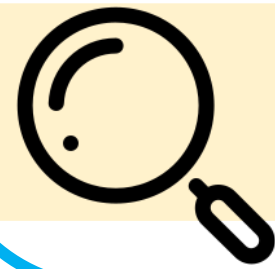
m = mass of 1 electron = $9 \times 10^{-31} \text{ kg}$



The properties of electron streams in a **MALtese cross** cathode ray tube



6 V heater is **SwitCh on**

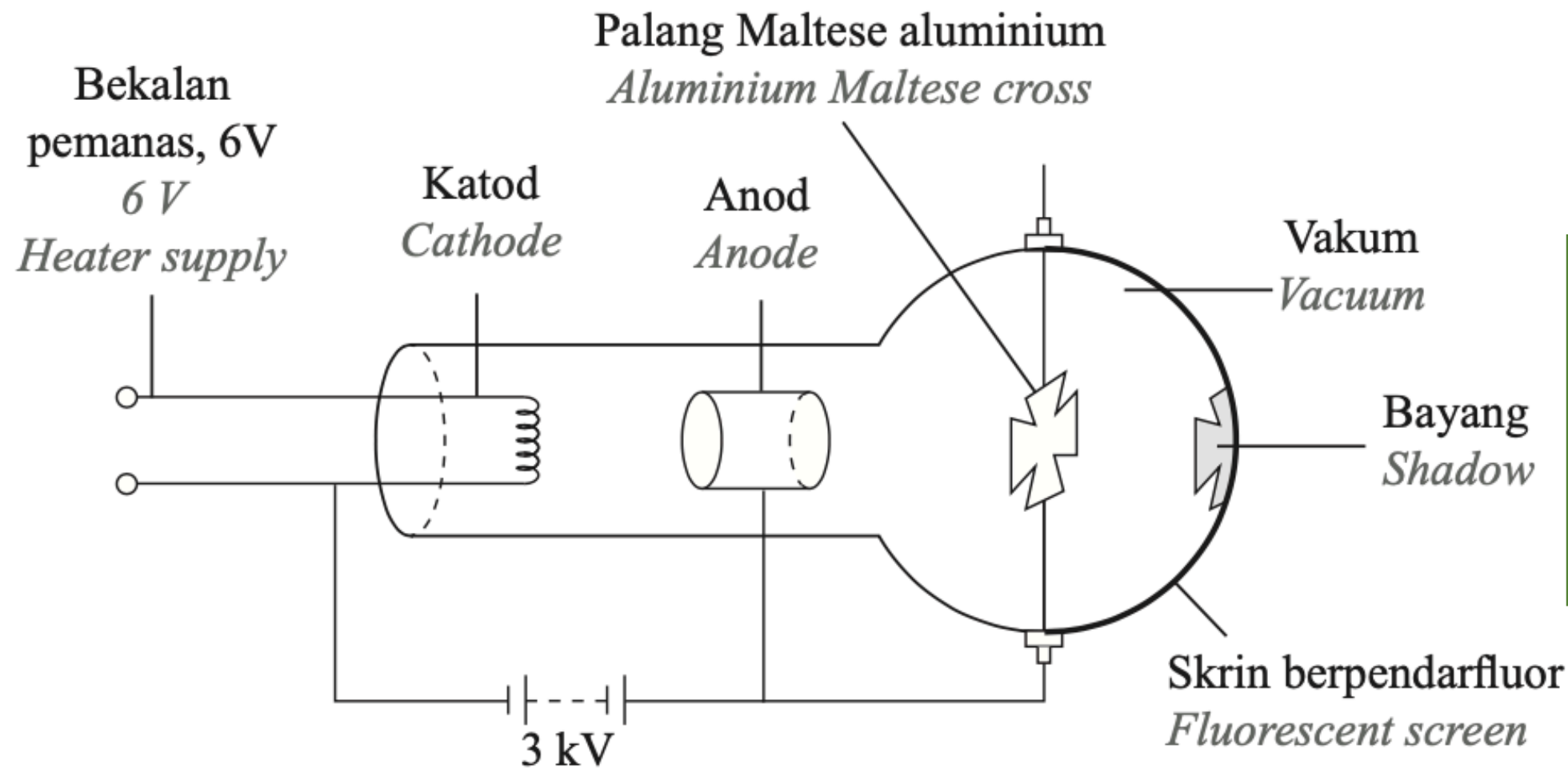


a **ShAdOW** of cross is seen

The **ShAdOW** is formed by the light rays from the **heated filament**

CONCLUSION: light rays travel in a **StRaight line**

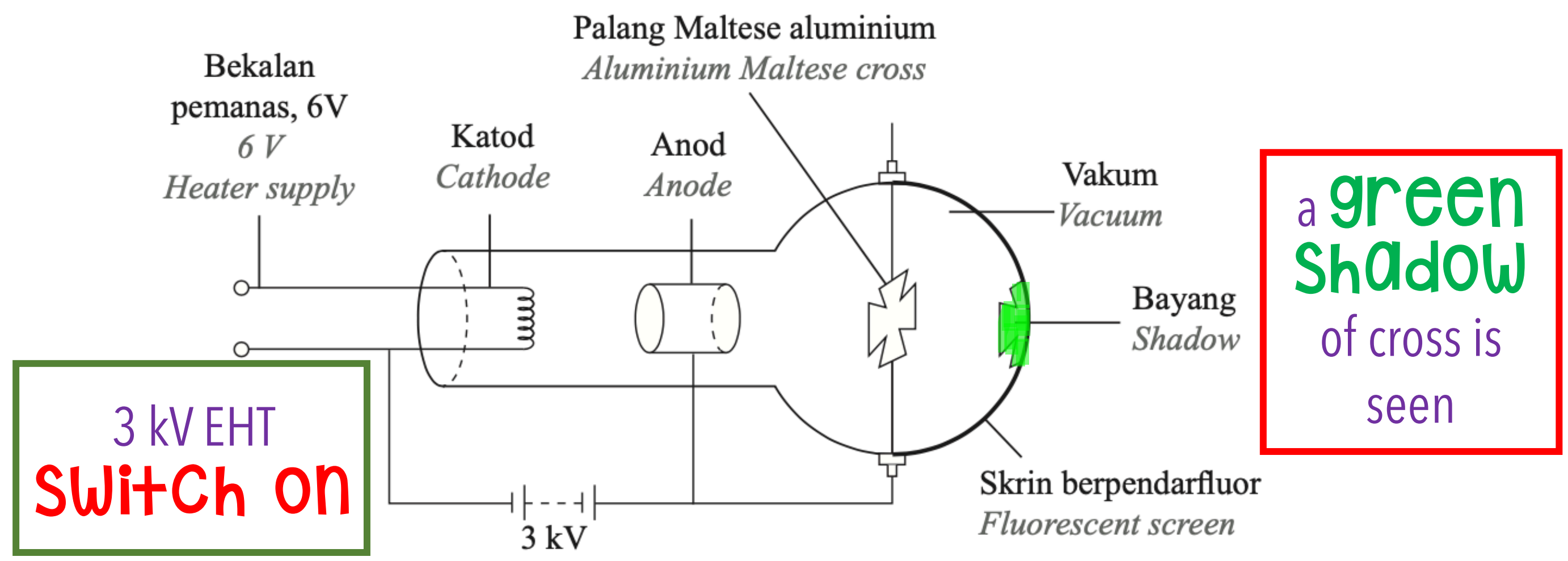
The properties of electron streams in a **Maltese cross** cathode ray tube




The **Shadow** is formed by the **Cathode rays**

Electrical energy → **Kinetic energy + light energy + heat energy**

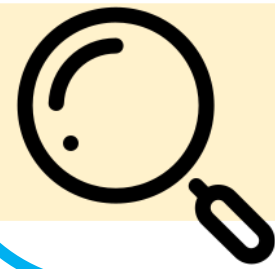CONCLUSION: Cathode rays cause fluorescence



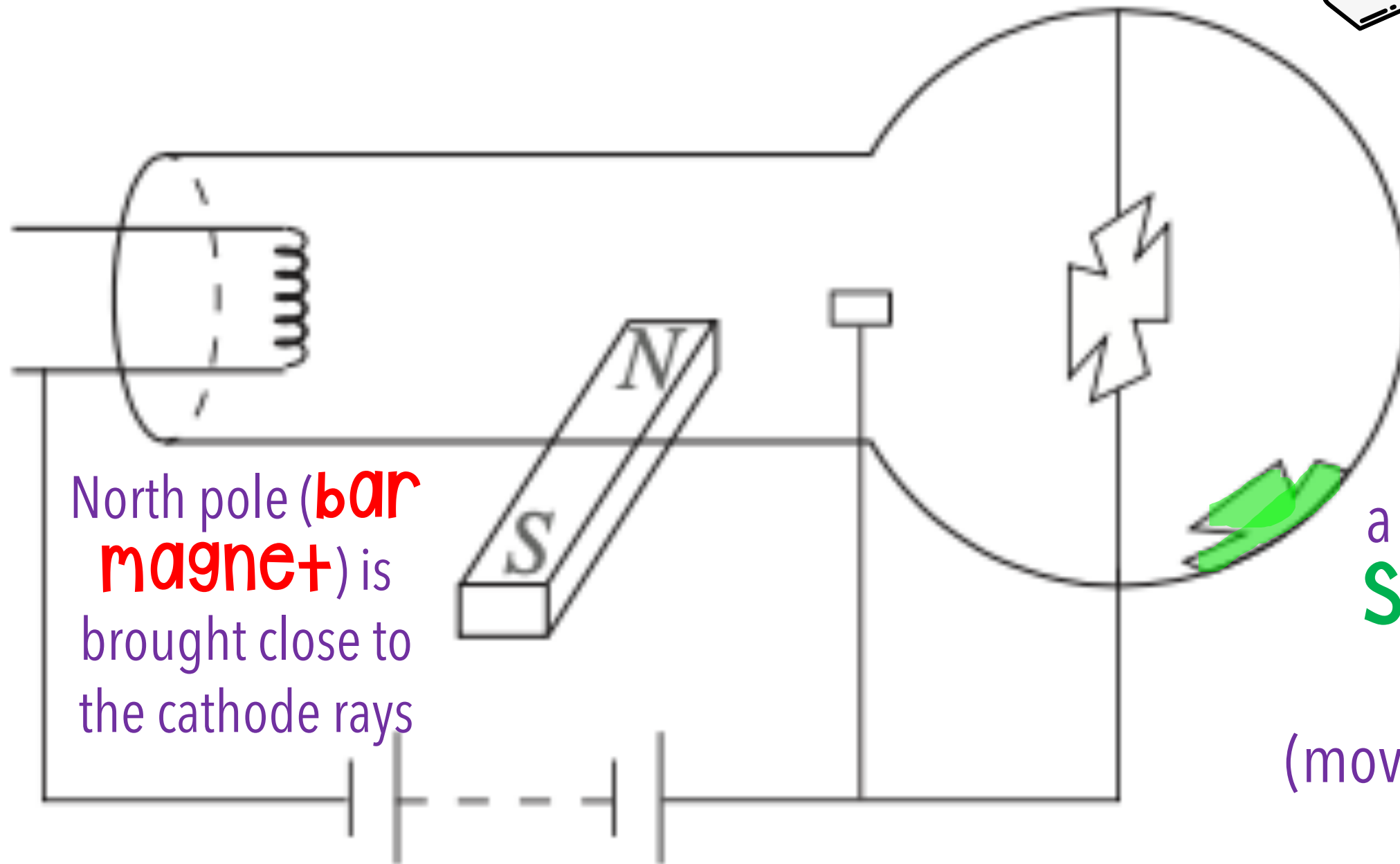The properties of electron streams in a **MATHESE CROSS** cathode ray tube




North pole (**bar magnet**) is brought close to the cathode rays

using **Fleming's left hand rule**

a **green shadow** distorted (move downwards)

CONCLUSION: **Cathode rays** can be deflected by **magnetic field**

Deflection tube

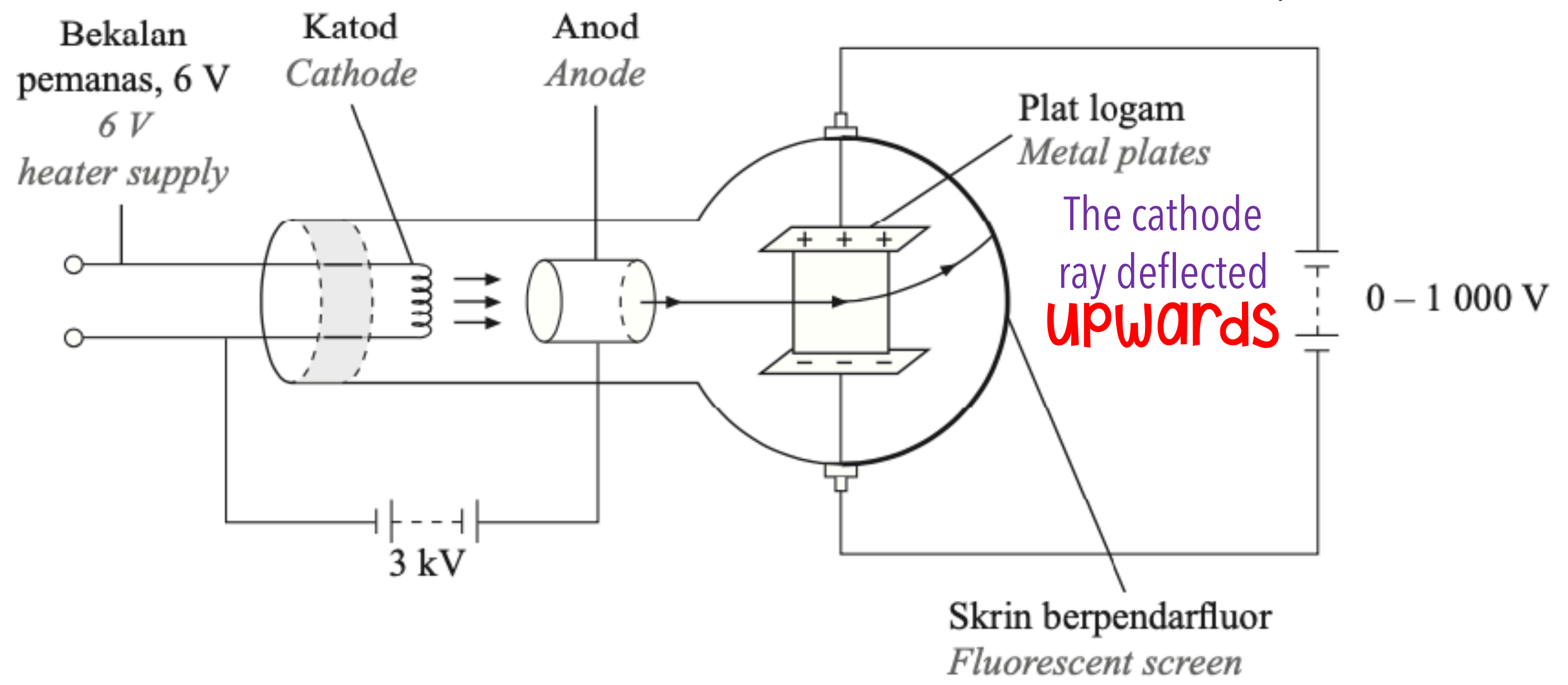


CONCLUSION: cathode rays **Negatively** charged
Cathode rays can be deflected by **electric field**



Uses of CATHODE RAY OSCILLOSCOPE



Vertical scale = Y-gain control

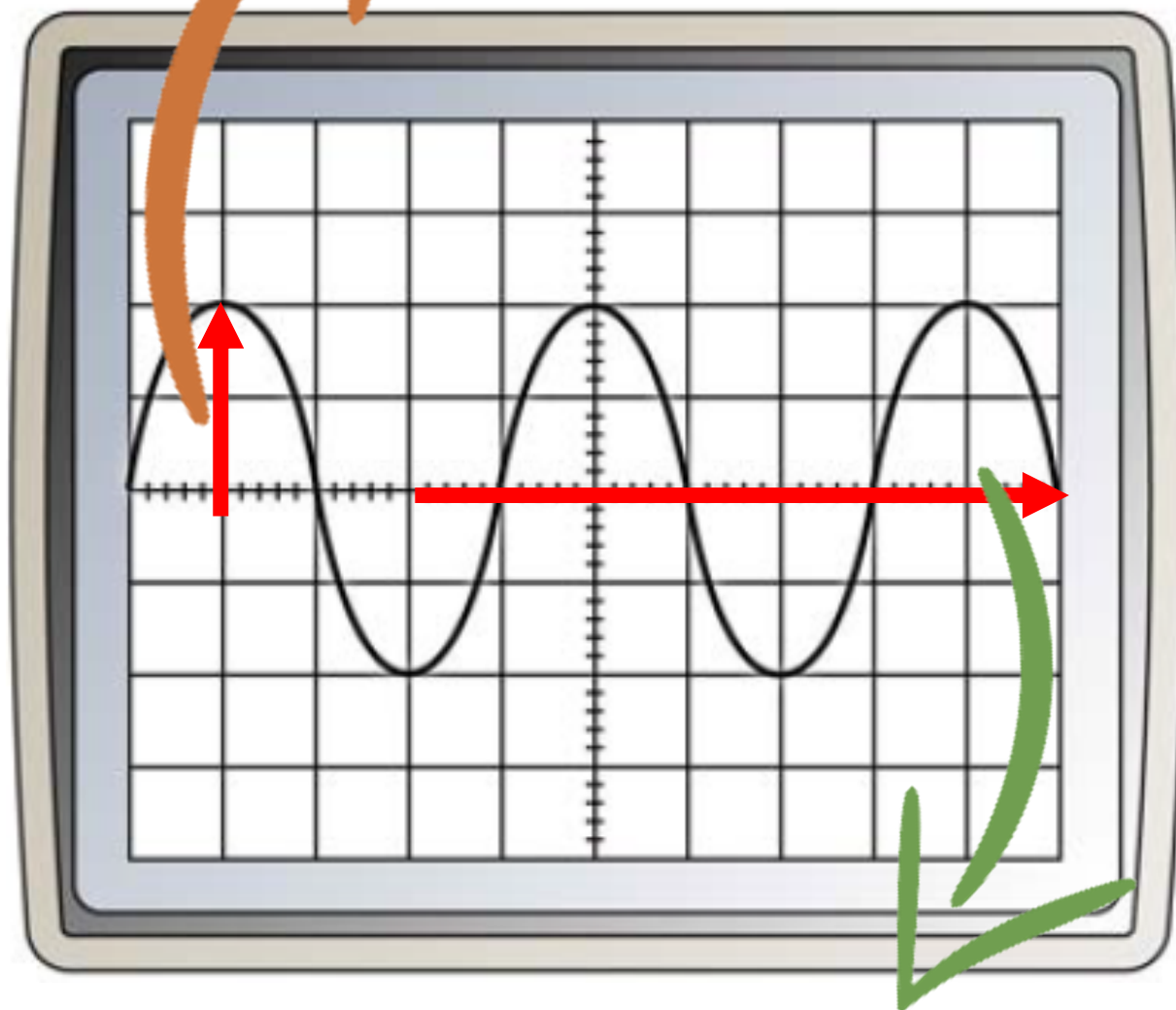

Horizontal scale = Time base

Period = time for 1
complete oscillation

Frequency,

$$f = \frac{1}{T}$$


The uses of cathode-ray oscilloscope are:

1. To measure a D.C or A.C voltage
2. To measure a short time intervals
3. To display the waveform

CATHODE RAY OSCILLOSCOPE

Display wave forms and measuring voltage from a DC source using a CRO







electronic

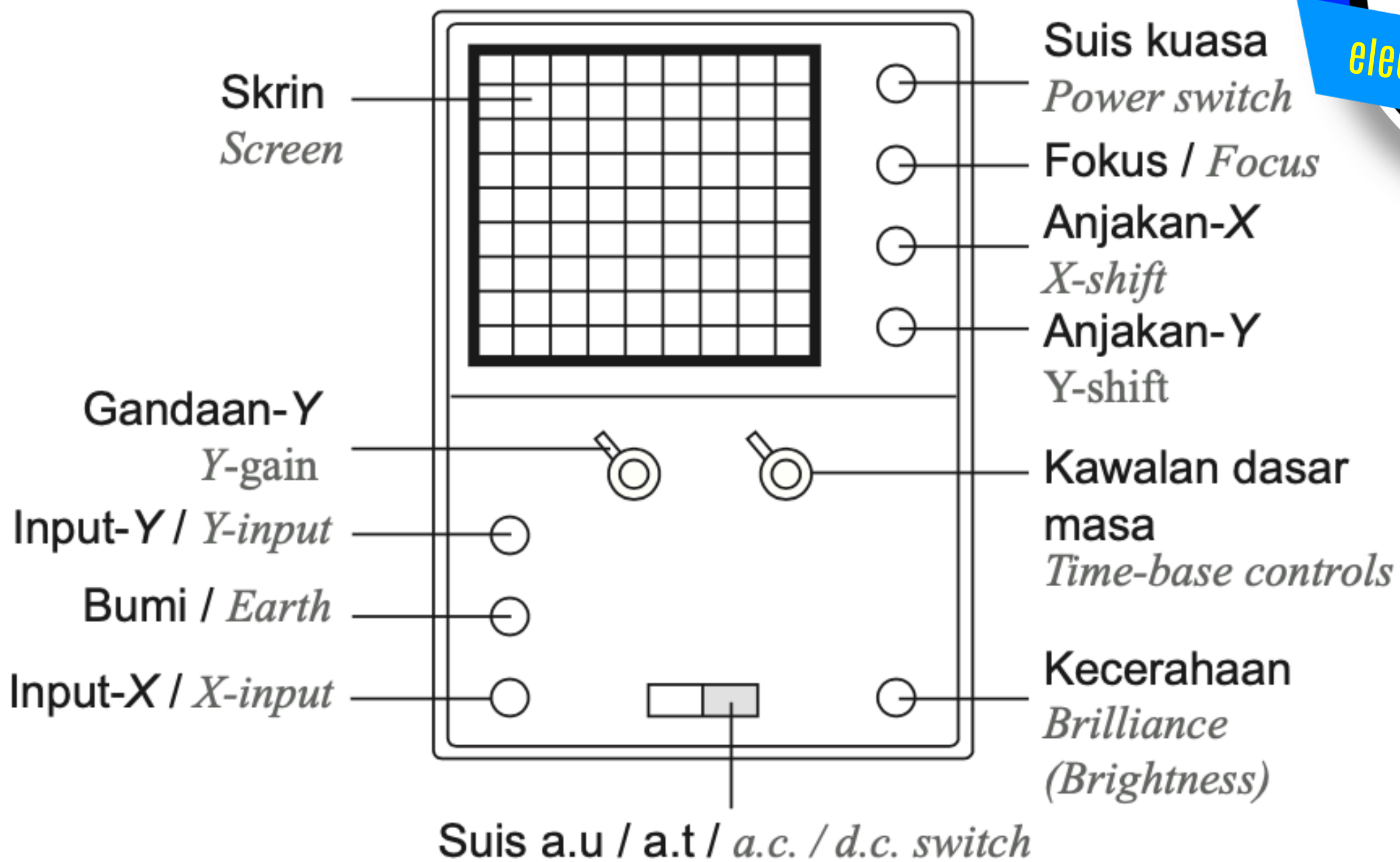

Cathode ray oscilloscope

Display wave forms and measuring voltage from a DC source using a CRO


electronic

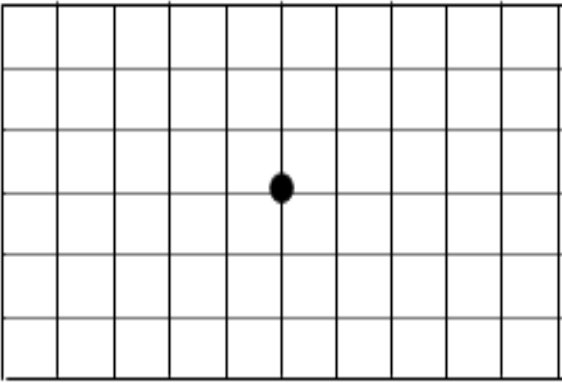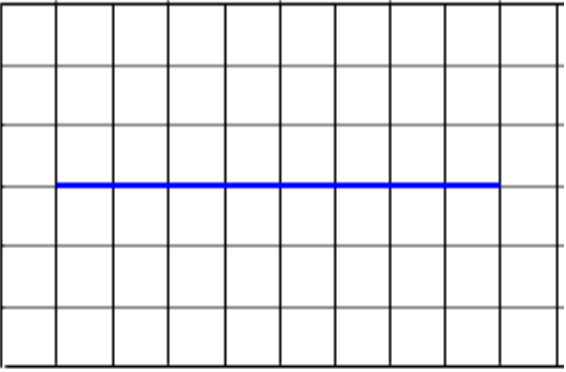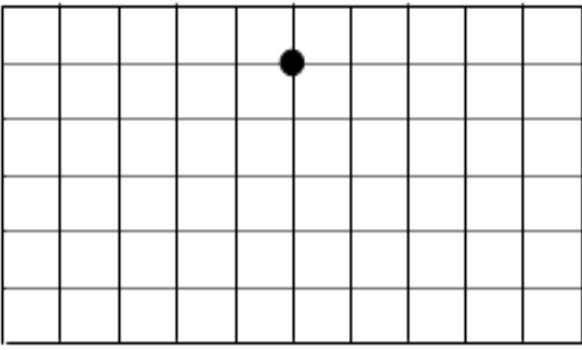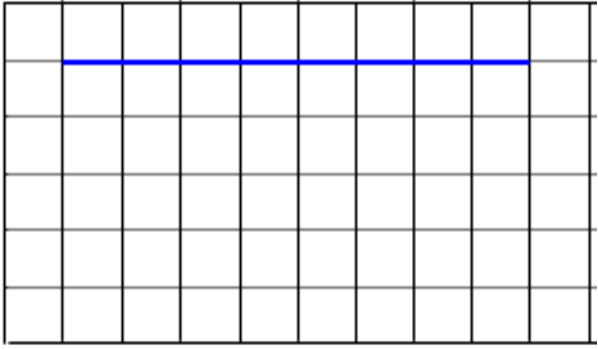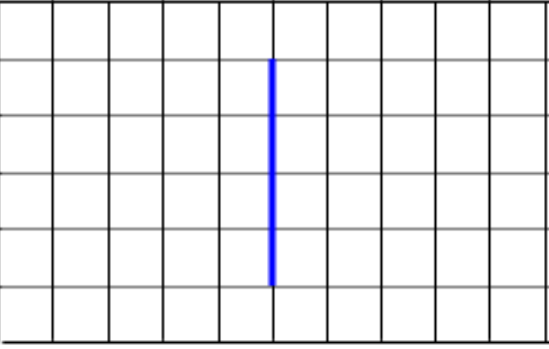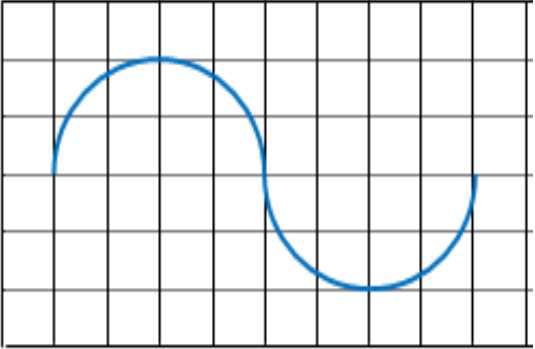Type of power supply connected to Y-input of CRO	Time-base switched Off	Time-base switched on
NO input		
DC power supply		
AC power supply		

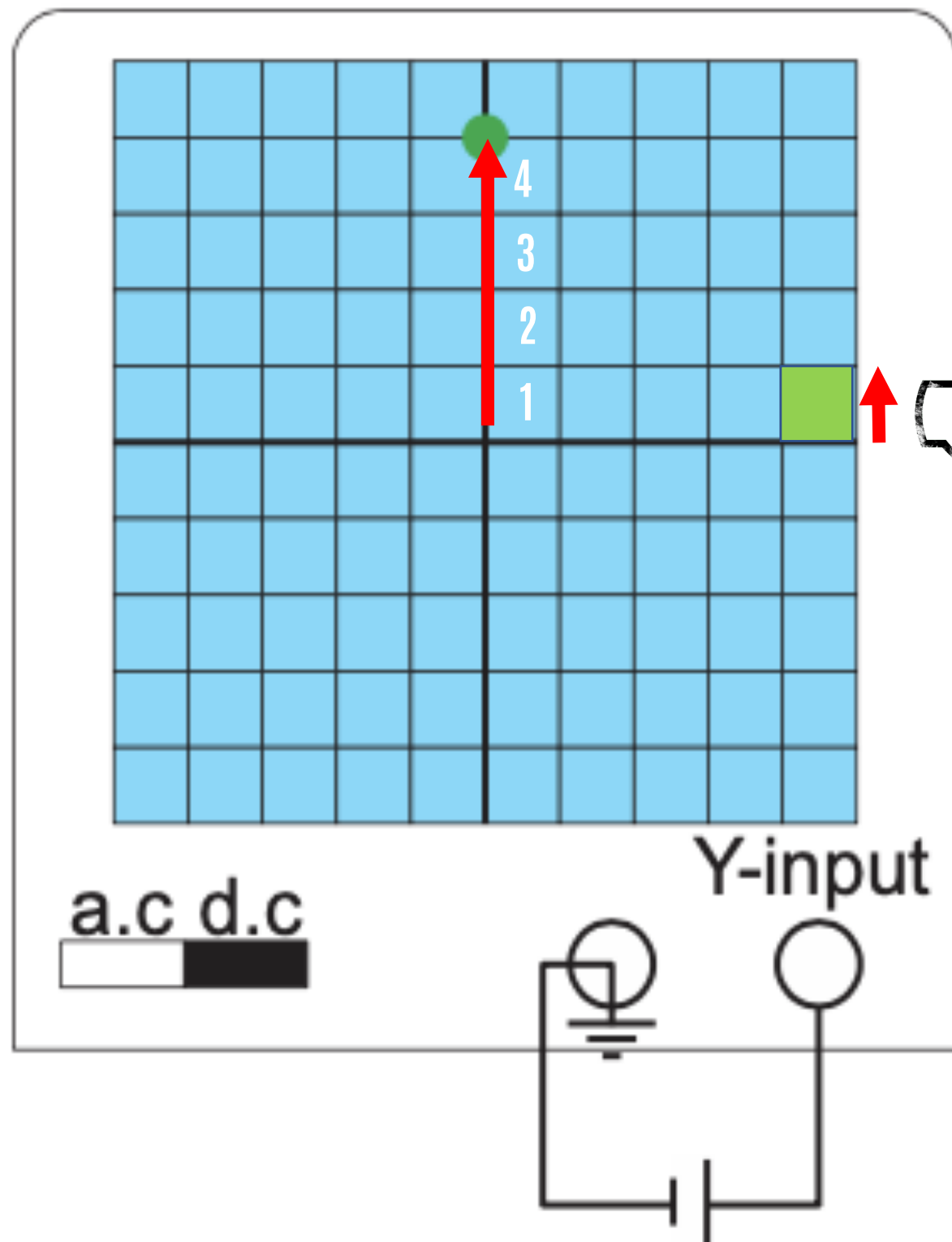example

Measuring Potential Difference using the CRO

What is the value of the **dc voltage** if the Y-gain control is **1 V/div** ?



Time-base switched **Off**


1 V /div

$$\begin{aligned} \text{dc voltage} &= 4 \text{ div} \times \frac{1 \text{ V}}{\text{div}} \\ &= 4 \text{ V} \end{aligned}$$

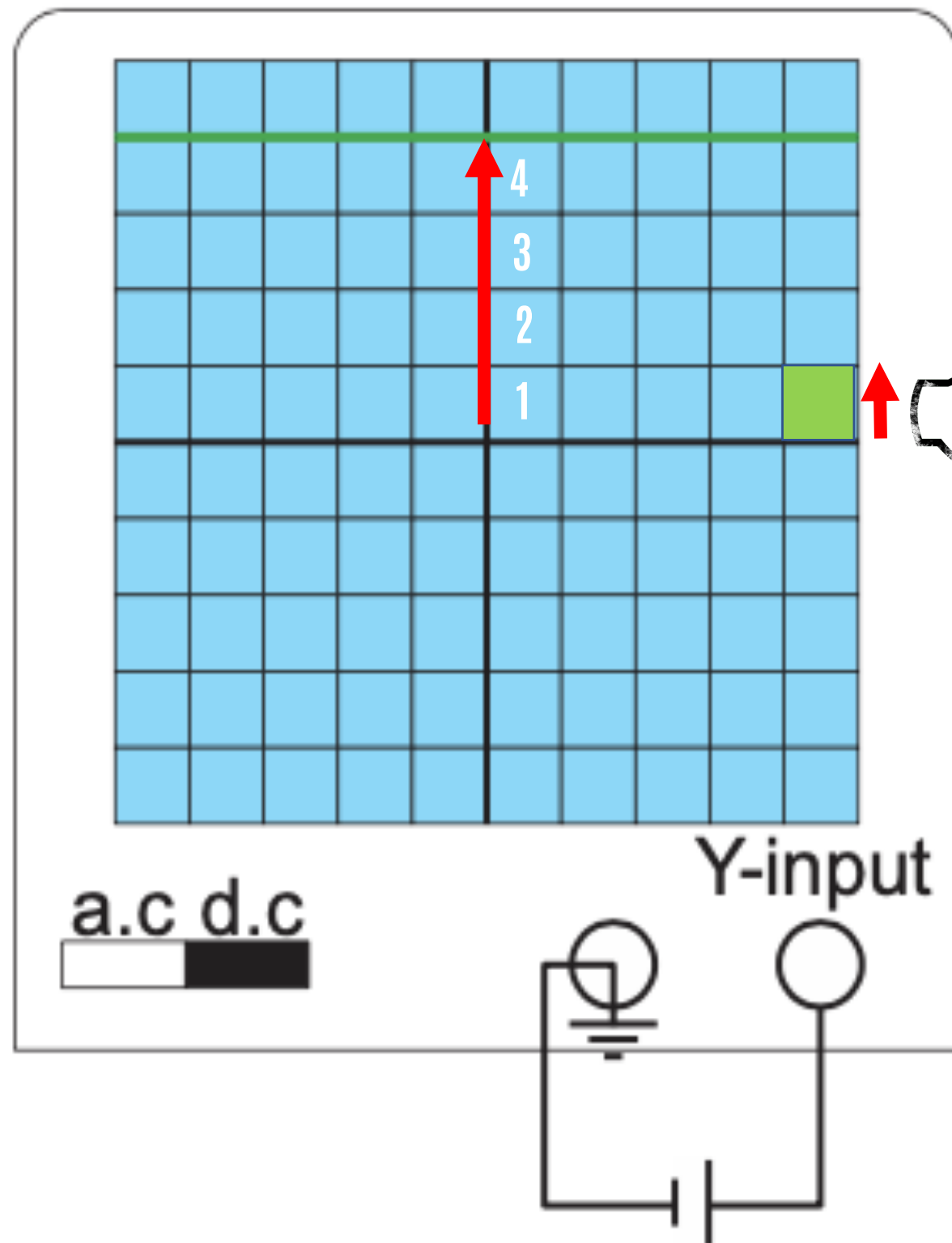example

Measuring Potential Difference using the CRO

What is the value of the **dc voltage** if the Y-gain control is **1 V/div** ?



Time-base switched **on**

1 V /div

$$\begin{aligned} \text{dc voltage} &= 4 \text{ div} \times \frac{1 \text{ V}}{\text{div}} \\ &= 4 \text{ V} \end{aligned}$$

example

Measuring Potential Difference using the CRO


Calculate the **PEAK VOLTAGE** and **PEAK TO PEAK VOLTAGE**.

Y-gain = 3 V/div

peak voltage

$$= 4 \text{ div} \times \frac{3 \text{ V}}{\text{div}}$$

$$= 12 \text{ V}$$

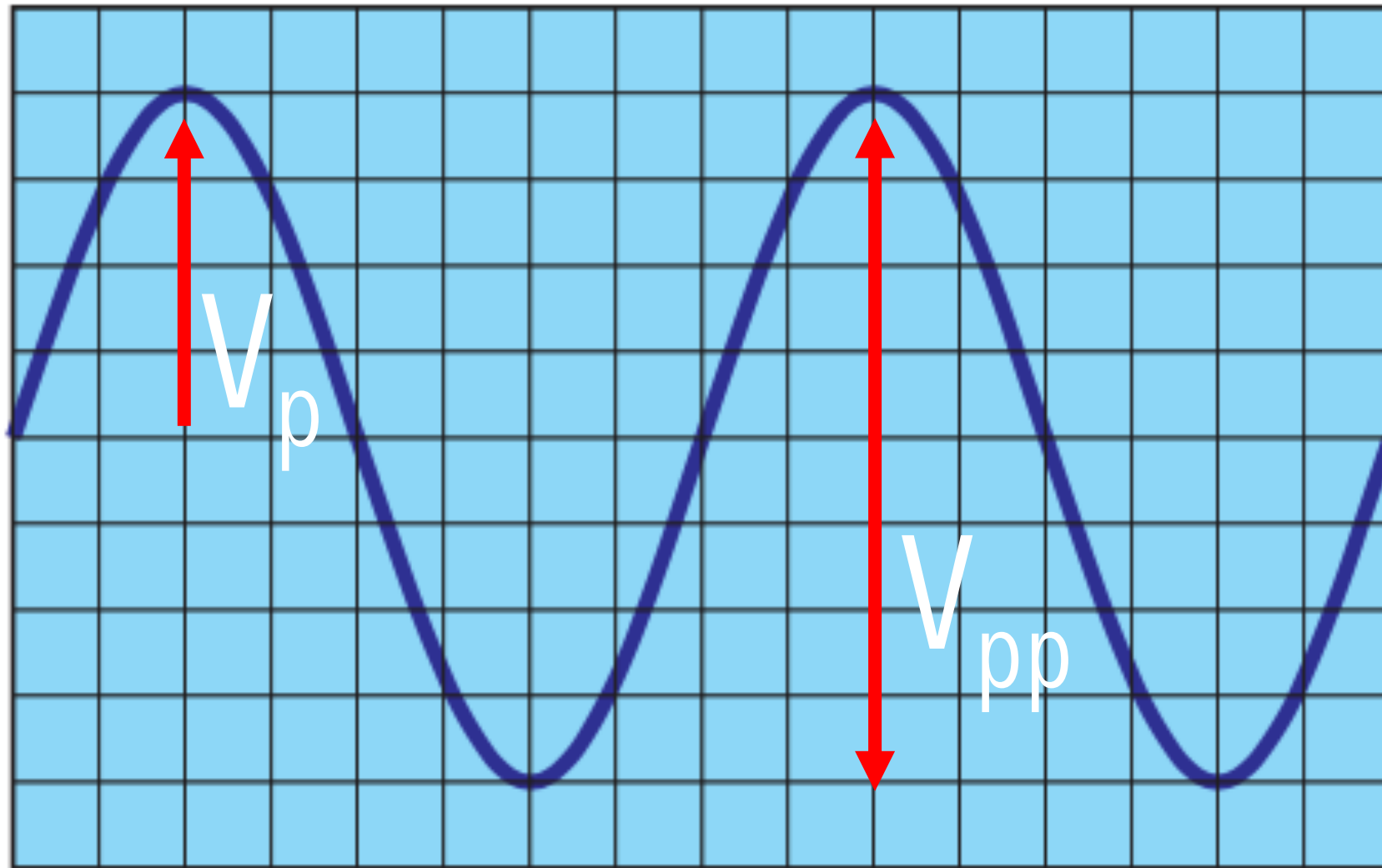


peak to peak voltage

$$= 8 \text{ div} \times \frac{3 \text{ V}}{\text{div}} = 24 \text{ V}$$

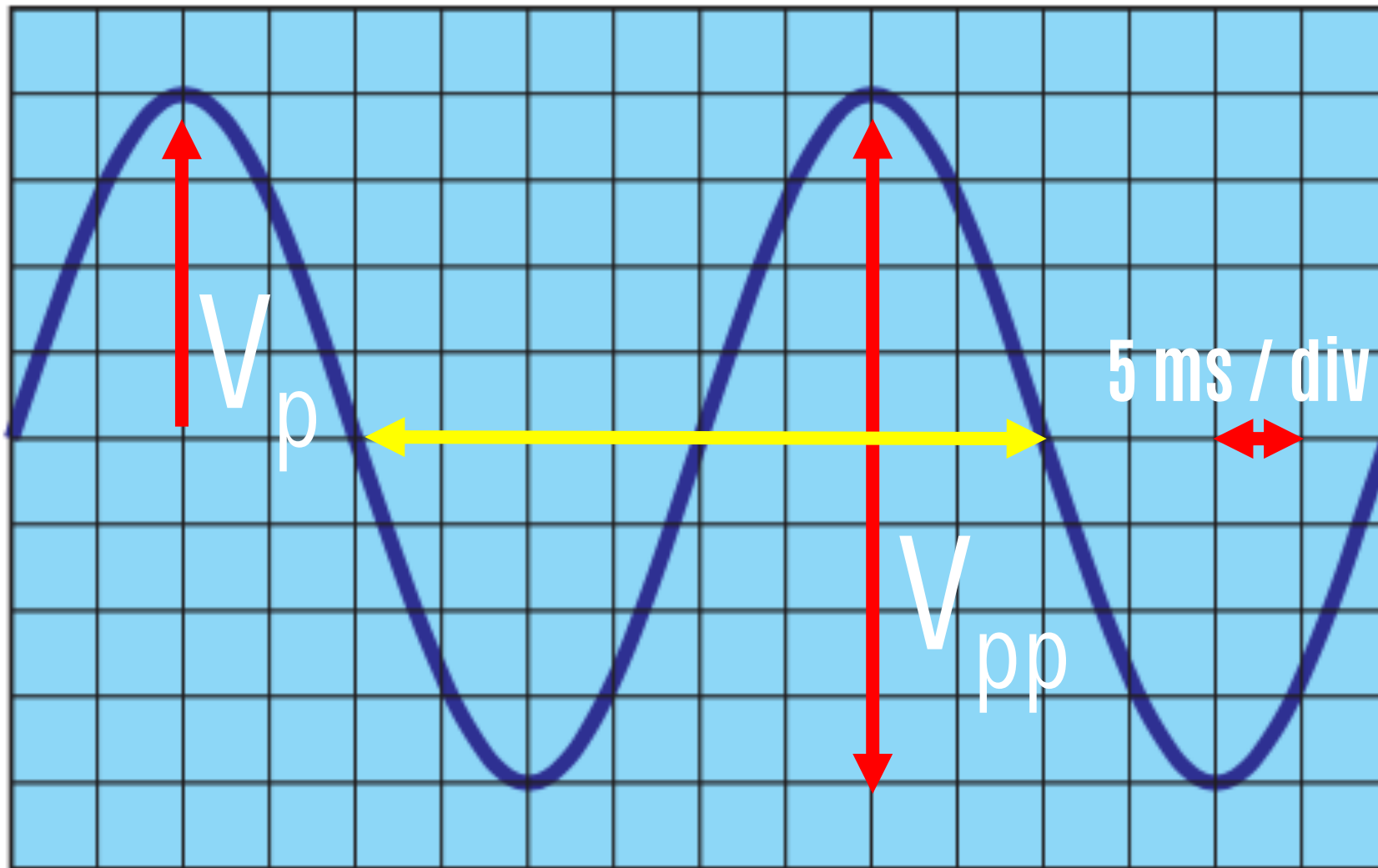example

Solve problems based on the CRO display

Y-input of an CRO setting at
20 V/div and 5 ms/div



$$\begin{aligned} & \text{peak voltage} \\ & = 4 \text{ div} \times \frac{20 \text{ V}}{\text{div}} = 80 \text{ V} \end{aligned}$$

$$\begin{aligned} & \text{peak to peak voltage} \\ & = 8 \text{ div} \times \frac{20 \text{ V}}{\text{div}} = 160 \text{ V} \end{aligned}$$

Period (T)

$$\begin{aligned} & = 8 \text{ div} \times \frac{5 \text{ ms}}{\text{div}} \\ & = 40 \text{ ms} = 4.0 \times 10^{-3} \text{ s} \end{aligned}$$


Frequency

$$= \frac{1}{T} = \frac{1}{4.0 \times 10^{-3}} = 25 \text{ Hz}$$

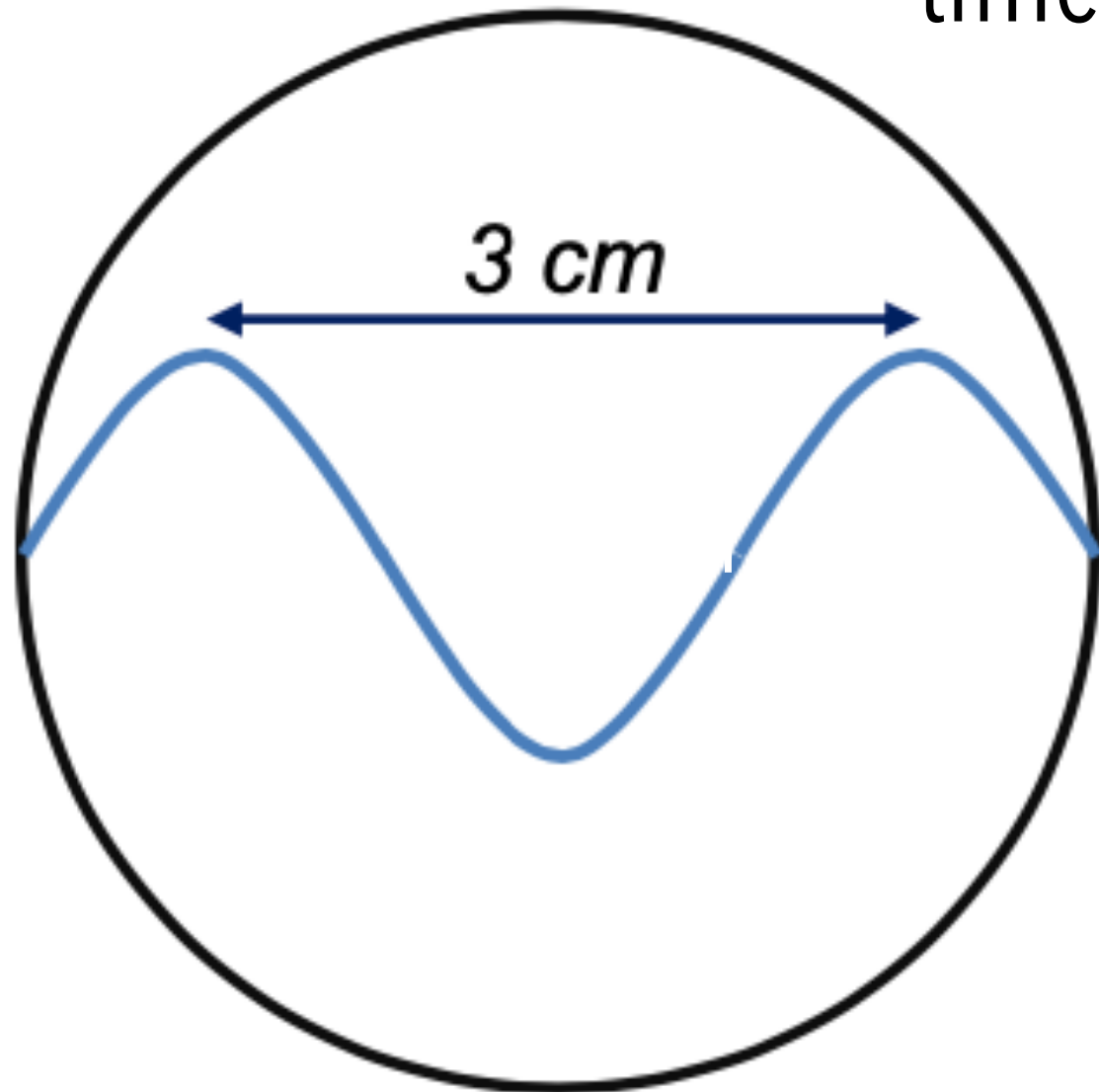example

Solve problems based on the CRO display

The length between the two crests is 3 cm.
(Given 1 division = 1cm)
time-base is set to 5 ms/div




Period (T)

$$\begin{aligned} &= 3 \text{ div} \times \frac{5 \text{ ms}}{\text{div}} \\ &= 15 \text{ ms} = 0.015 \text{ s} \end{aligned}$$

Frequency

$$= \frac{1}{T} = \frac{1}{0.15} = 66.67 \text{ Hz}$$

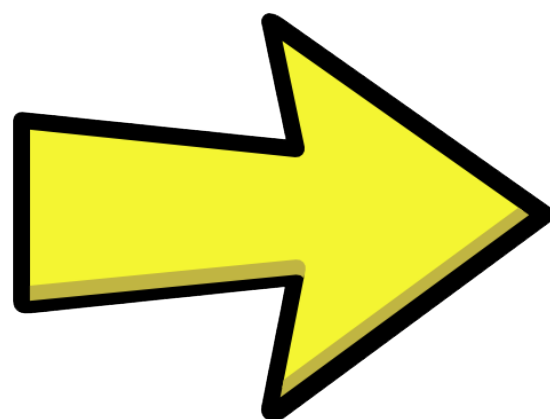When the frequency of the wave is double, what is the length between the two crests?




Frequency double (2 times)
 \therefore Period decrease (2 times)

$$\text{Length} = \frac{3}{2} = 1.5 \text{ cm}$$

semiconductor

characteristic


as **insulator** at

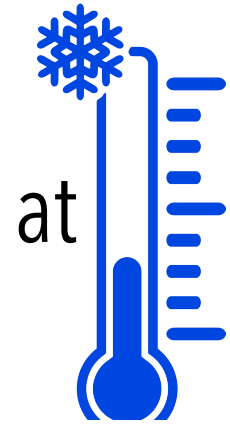

has **good electrical conductivity** at





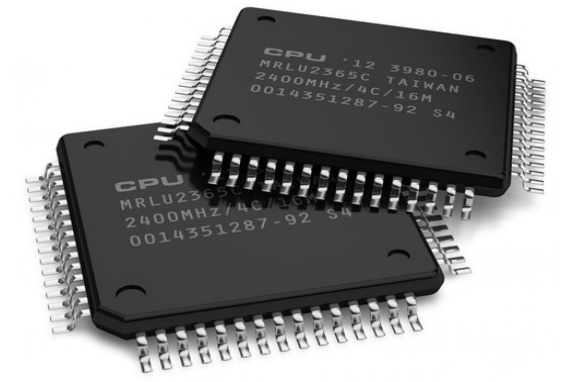material that has **electrical conductivity** that is **between** that of a **conductor** and an **insulator**



Example of semiconductor are:

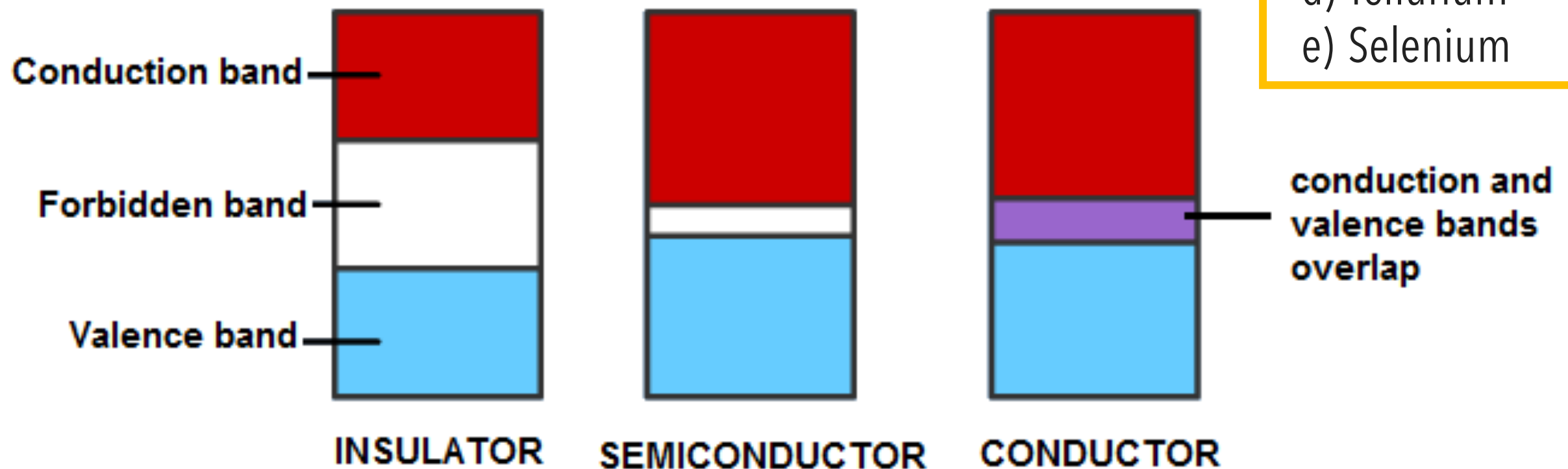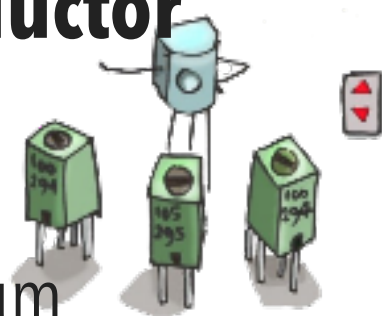- a) Silicon
- b) Germanium
- c) Boron
- d) Tellurium
- e) Selenium



Comparison between **energy gap** in insulator, semiconductor and conductor

a process of adding a small amount of **impurities** to a semiconductor

doping

5N APA

5 → **pentavalent**
N → **n-type**

Doping material → A = Antimony
P = Phosphorus
A = Arsenic

Role of doping material → atom **donor**
Majority charge carrier → **free electrons**
Minority charge carrier → **holes**

free electrons carry **negative** charge
holes carry **positive** charge



electron moving to the left = 'holes' moving to the right

3P BAGI


3 → **trivalent**
P → **p-type**

Doping material → B = Boron
A = Aluminium
G = Gallium
I = Indium

Role of doping material → atom **receiver**
Majority charge carrier → **holes**
Minority charge carrier → **free electrons**



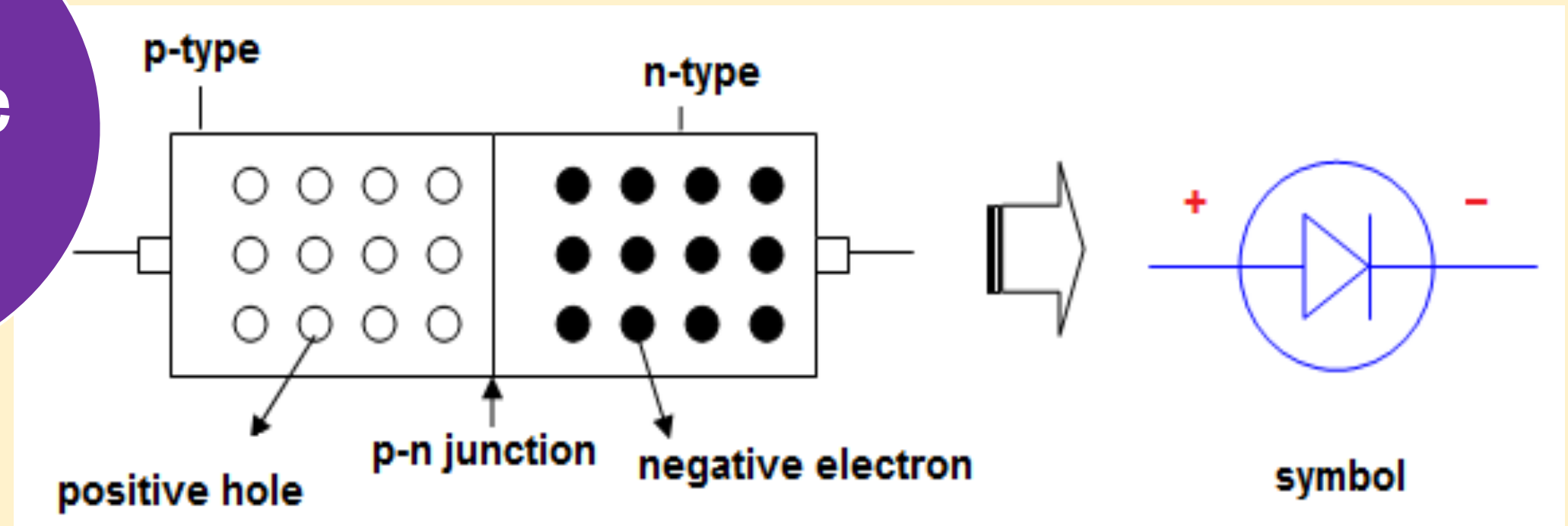
Semiconductor diode is to allow current to flow through it in **one direction** only
HOW?




DEPLETION layer

neutral region which has **no charge carriers** and **poor conductor of electricity**

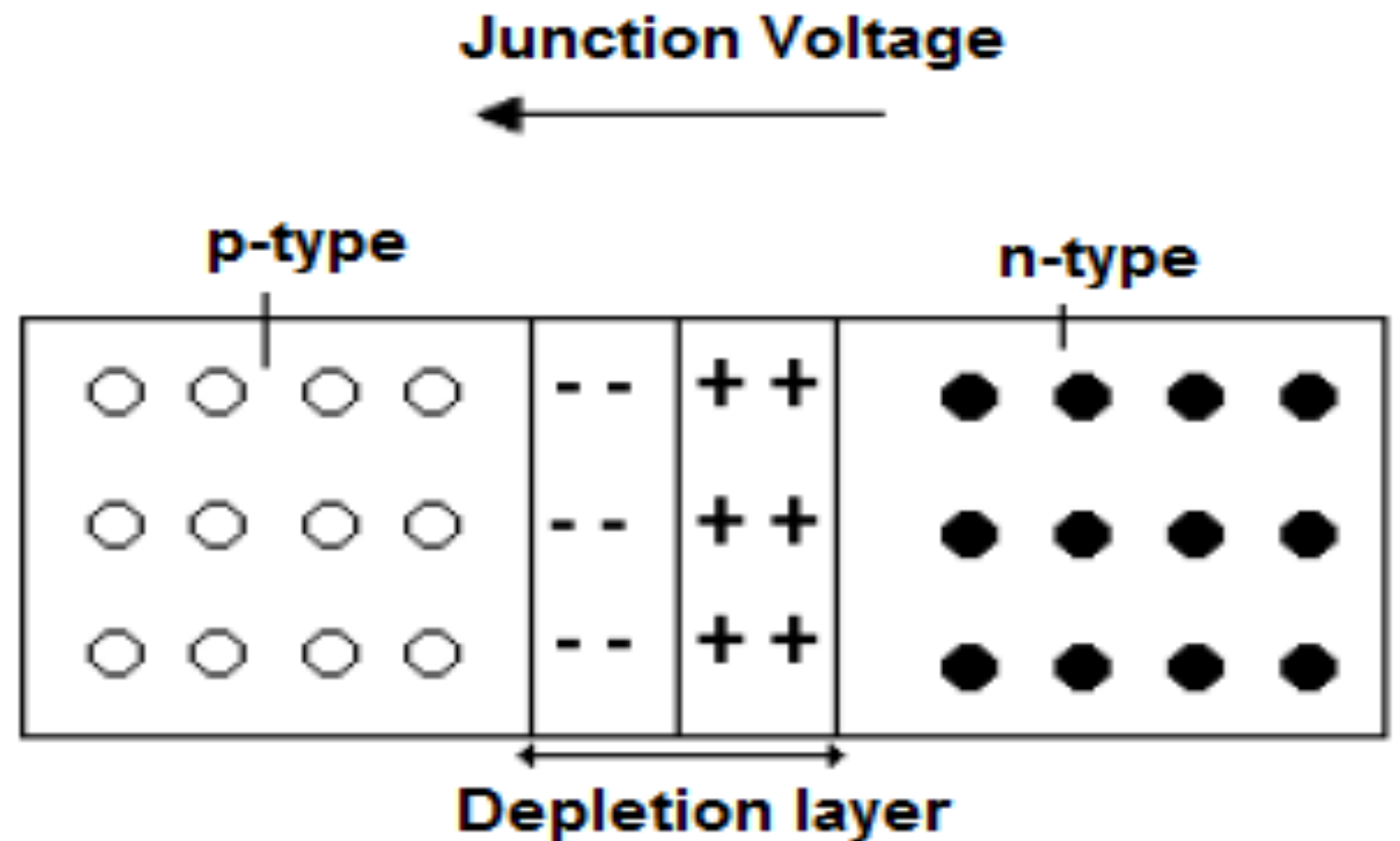The **Wider** the depletion layer, **no current** flow



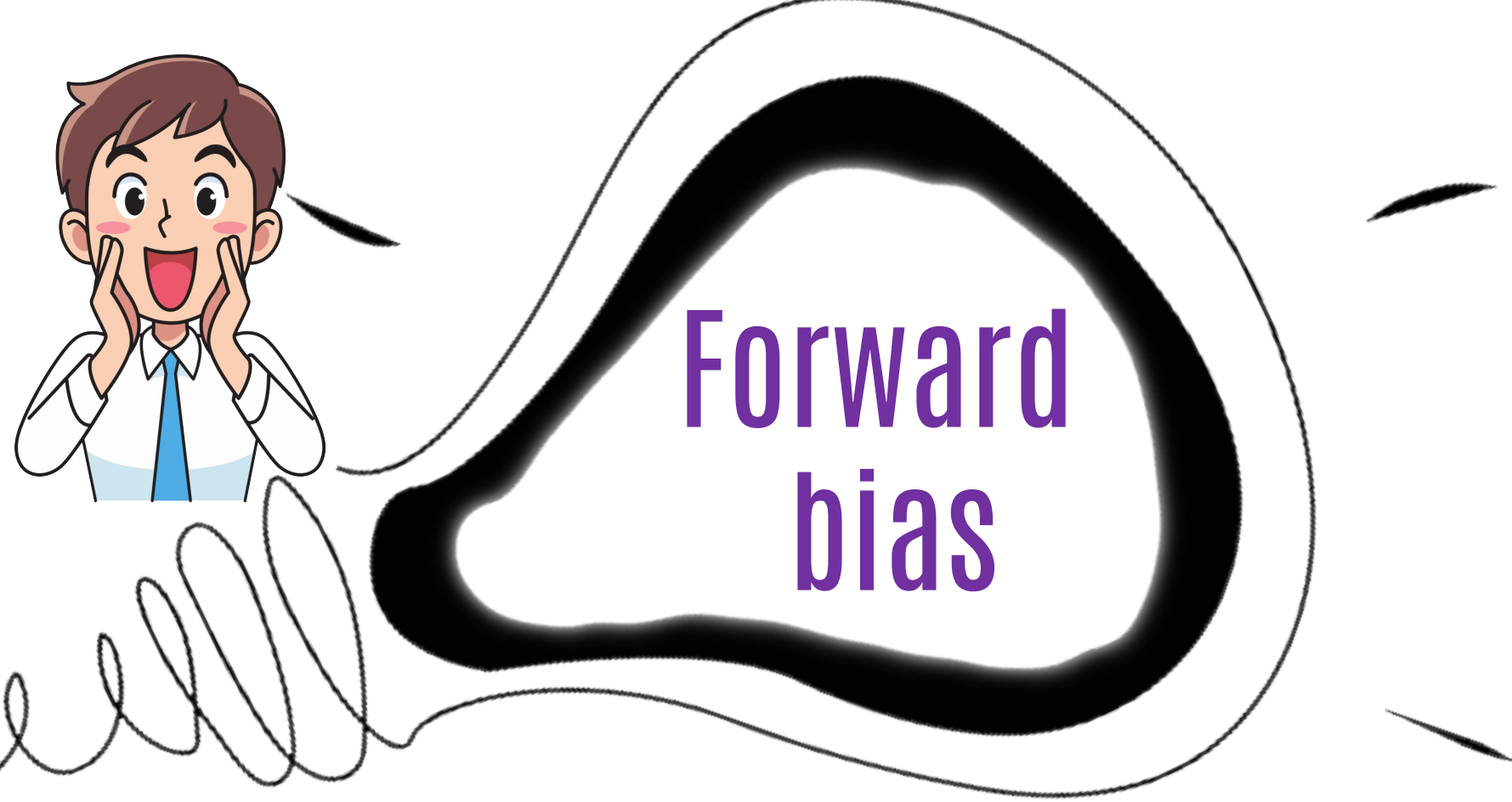


Forward bias



n-type semiconductor is connected to **negative dry cell**

Depletion layer is **narrow**
(resistance diode decrease)

current flow

Bulb **light up**

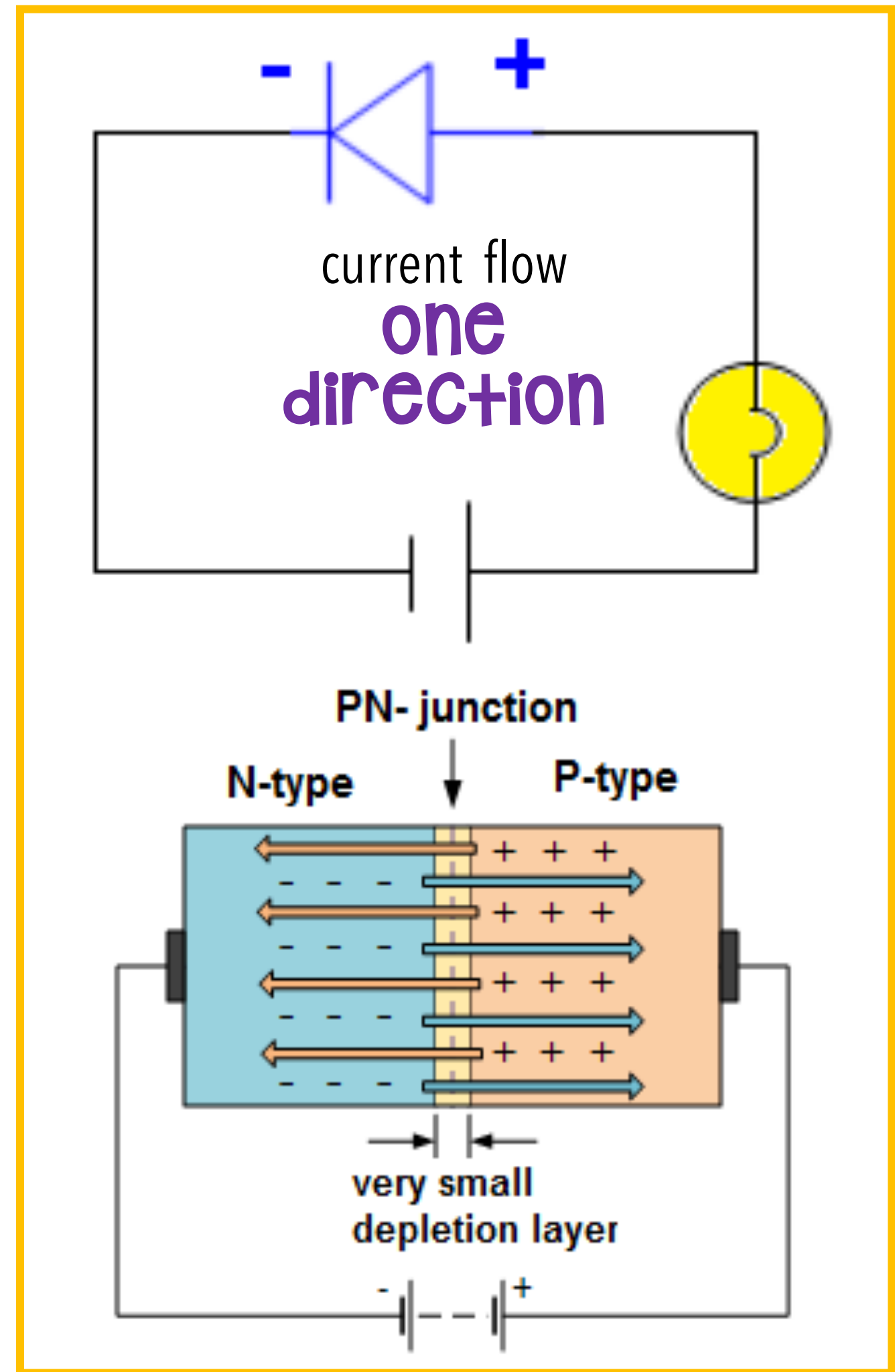

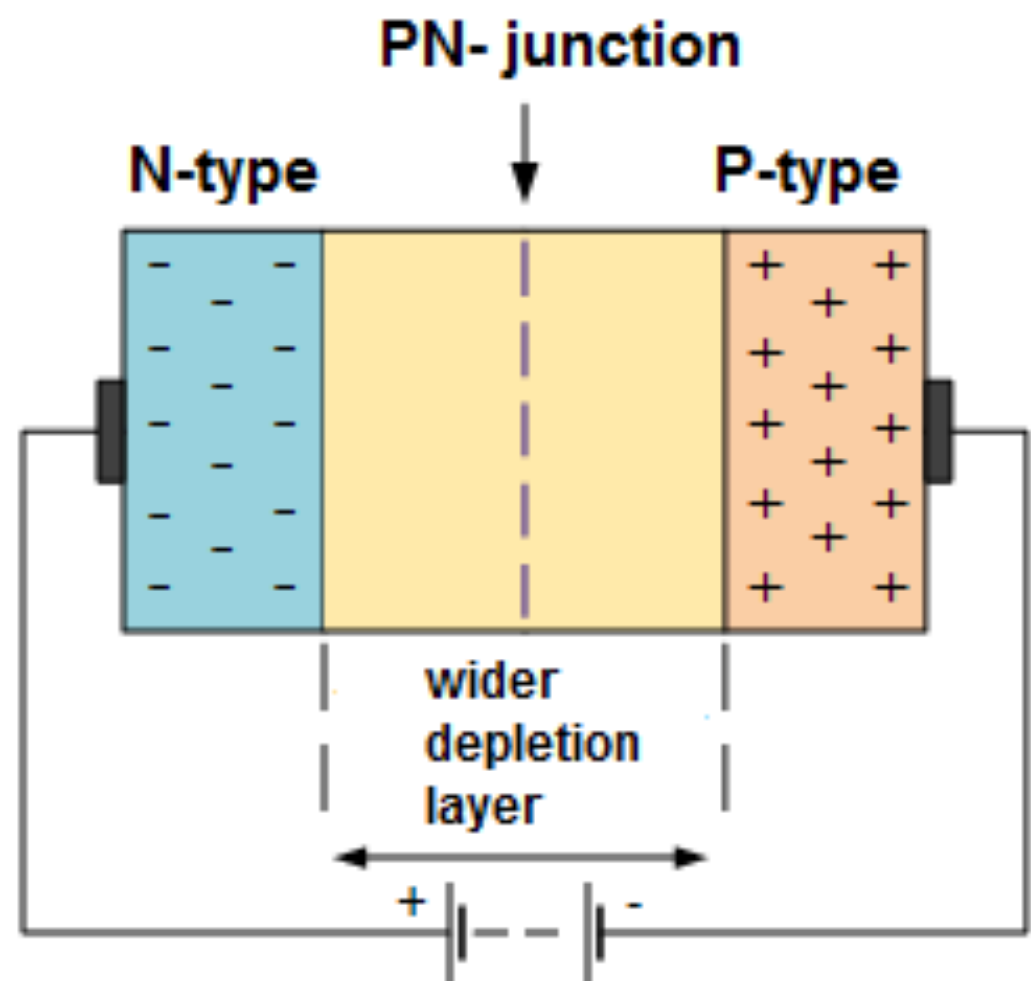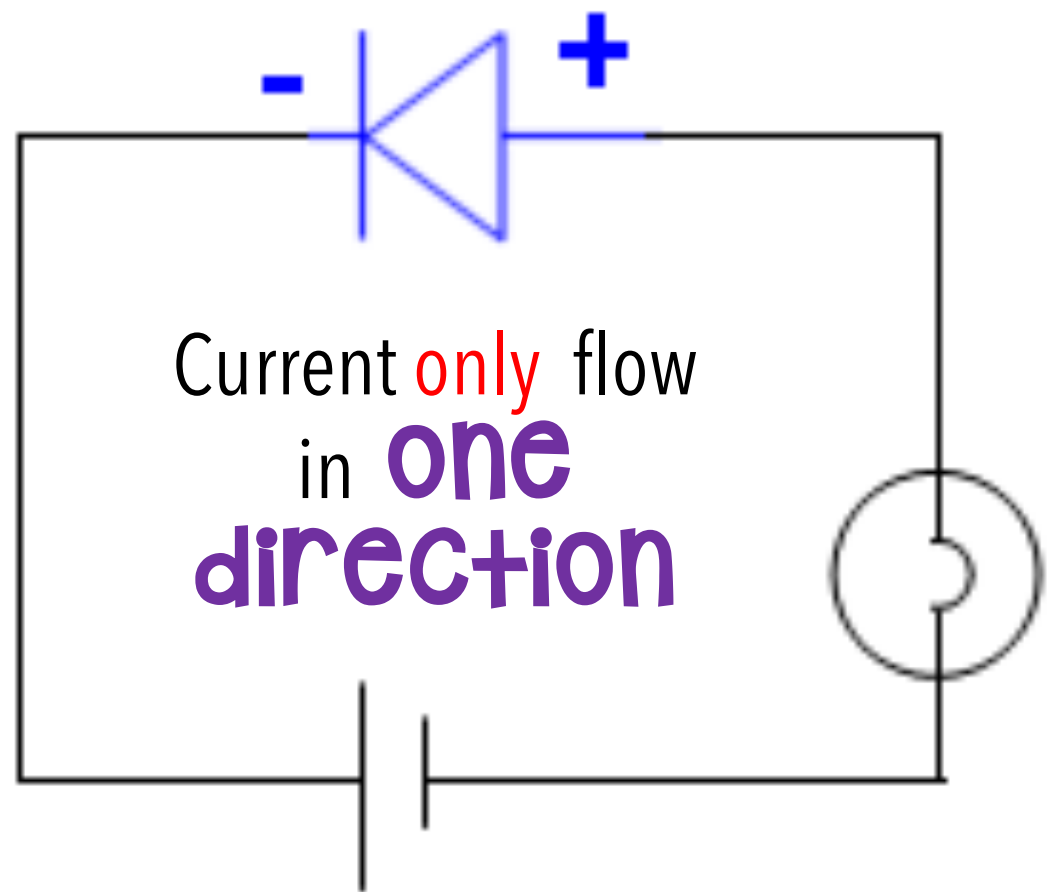

Reverse
bias



n-type semiconductor is connected to **POSITIVE DRY CELL**


DEPLETION layer is **wide**
(resistance diode increase)

NO CURRENT FLOW

Bulb **NOT LIGHT UP**

Rectification is a process to **convert** an **alternating current** into a **direct current** by using a **diode**

Half wave
rectification

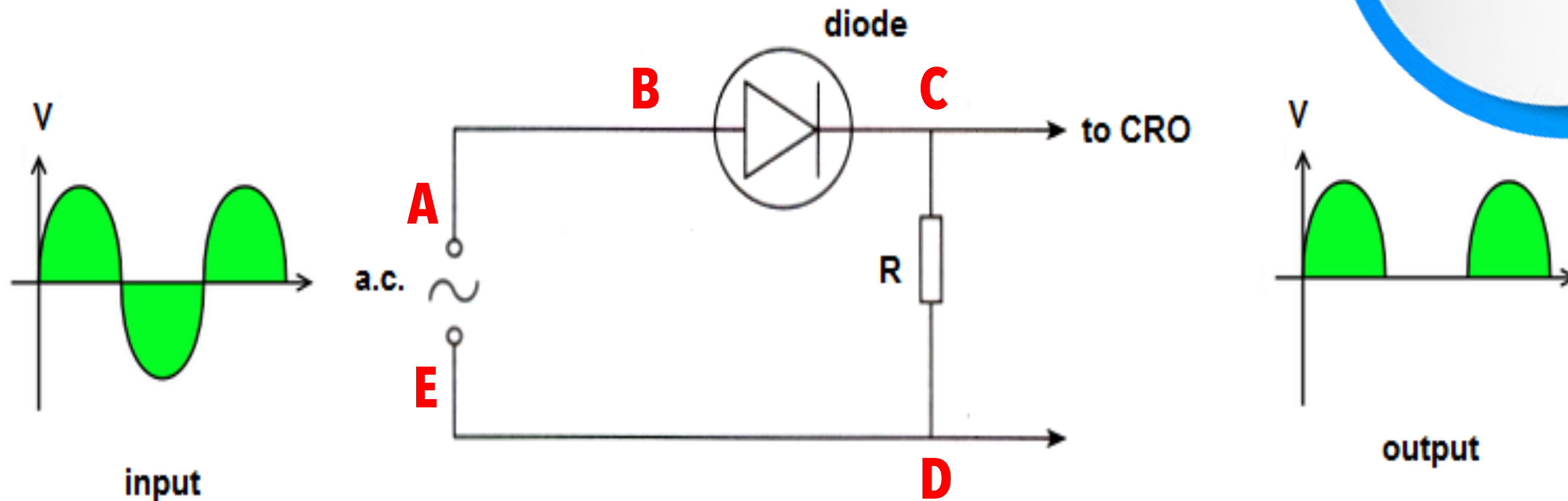


current will only flow in the first half-cycle when the diode is in **forward bias** ($A \rightarrow B \rightarrow C \rightarrow D \rightarrow E$)

The current is blocked in the second half-cycle when the diode is in **reverse bias** ($E \rightarrow D \rightarrow C \rightarrow B \rightarrow A$)

Rectification is a process to convert an alternating current into a direct current by using a diode

FULL
Half Wave
rectification

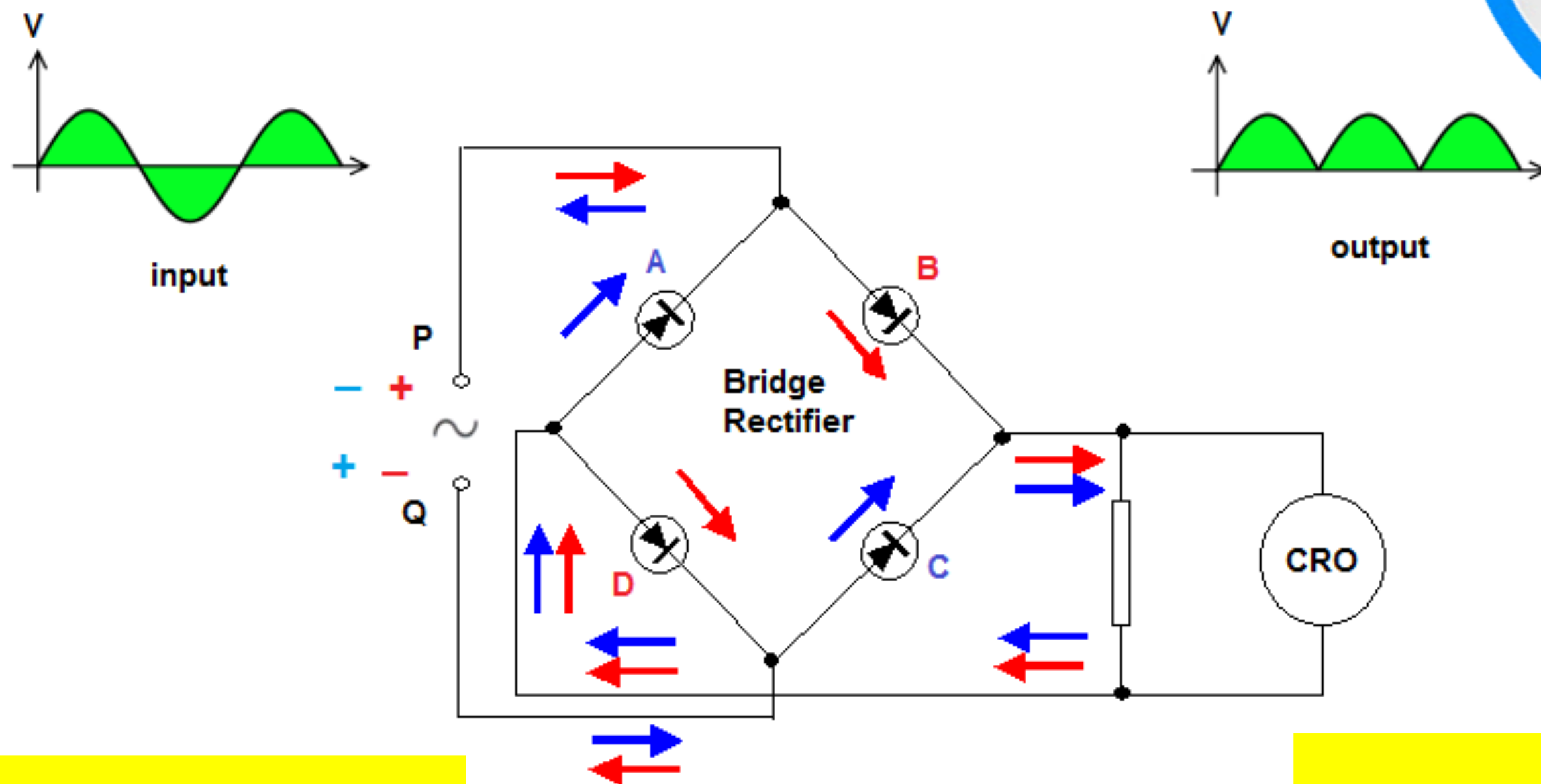

In the first half, the current flows from $P \rightarrow B \rightarrow D \rightarrow Q$

keyword:
RED = first half cycle
BLUE = second half cycle

In the second half, the current flows from $Q \rightarrow C \rightarrow A \rightarrow P$


The uses of capacitor

When the **current** pass through the resistor and capacitor, the **capacitor is charged** and stores energy.


When there is **no current** pass through the resistor and capacitor, the **capacitor discharge**

The energy from it is used to produce voltage across the resistor.

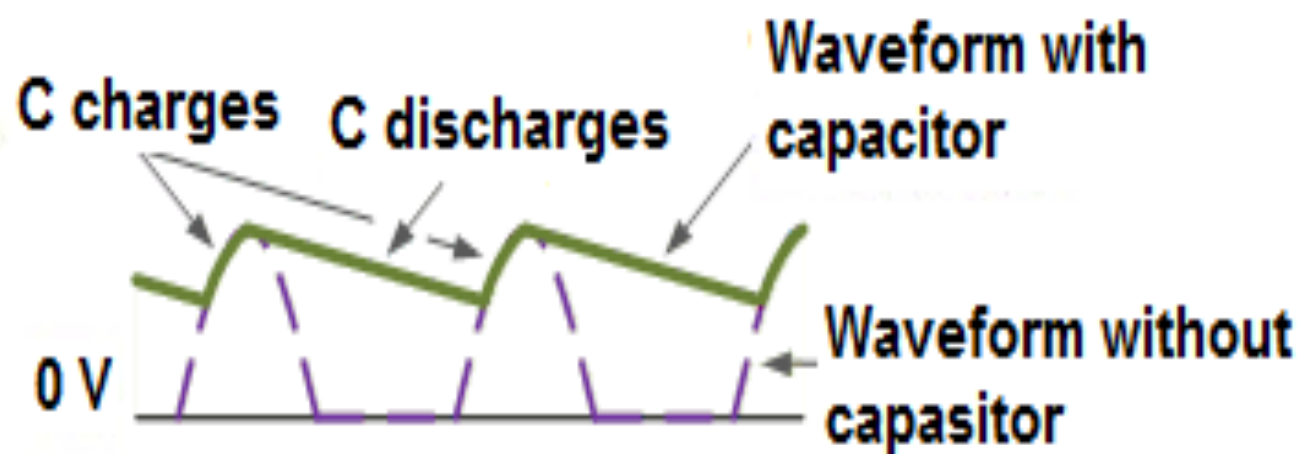As a result it produces a **smooth dc output**



half-wave

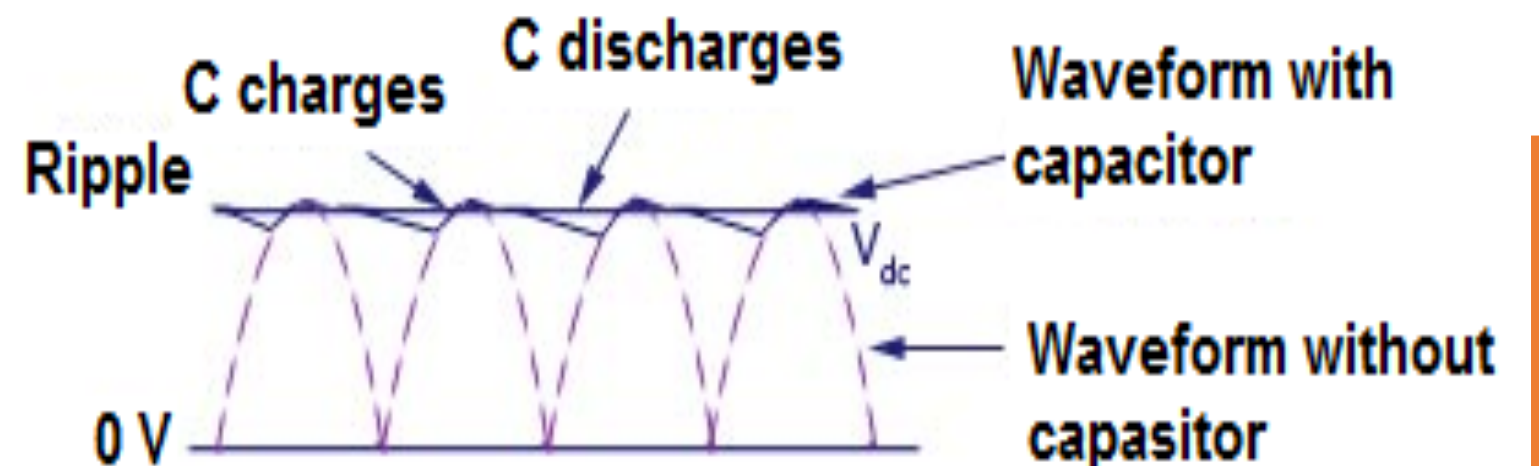


full-wave


transistor

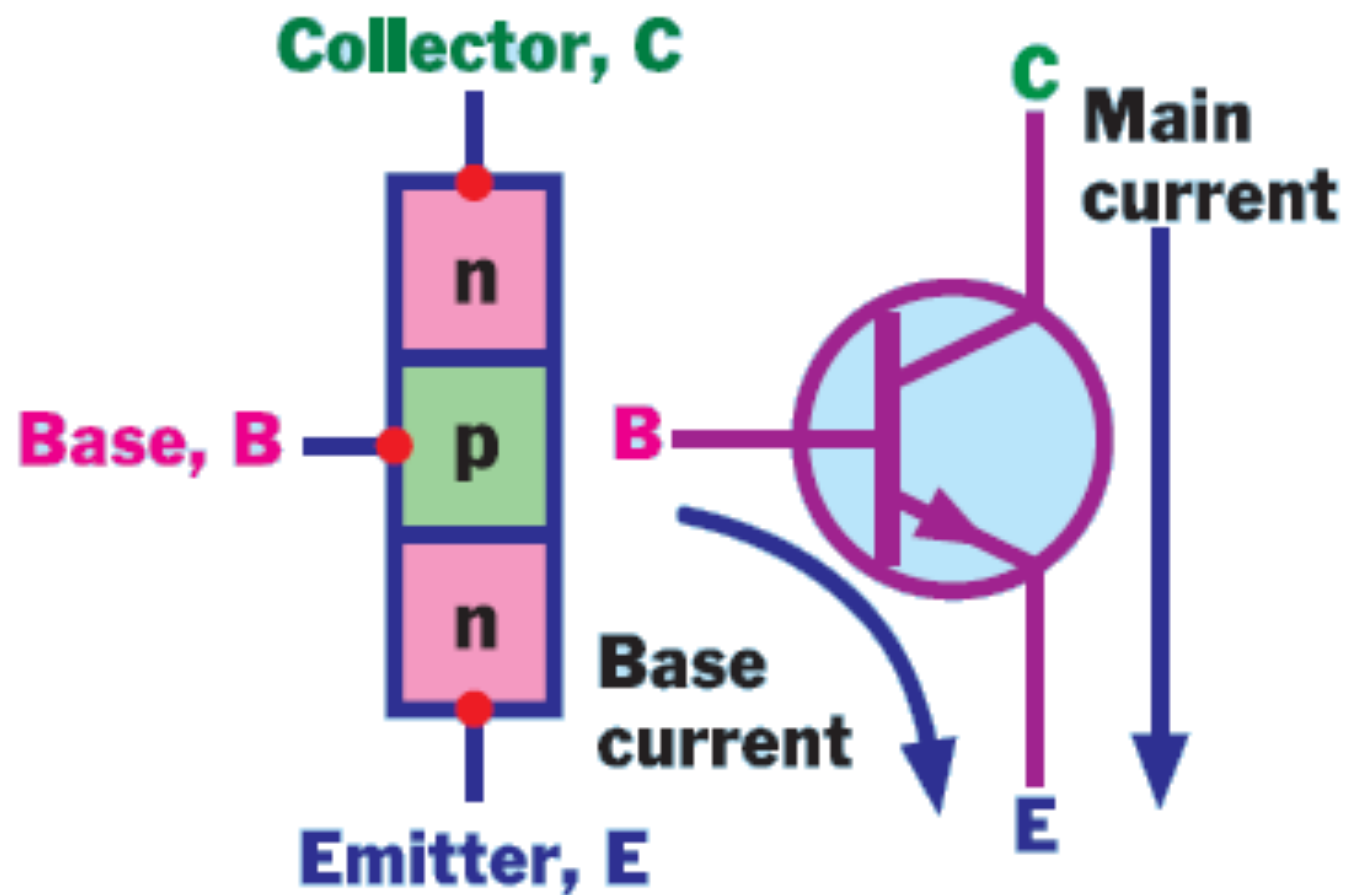4.3

To **amplify** the **current**
or act as a **Switch**



npn transistor

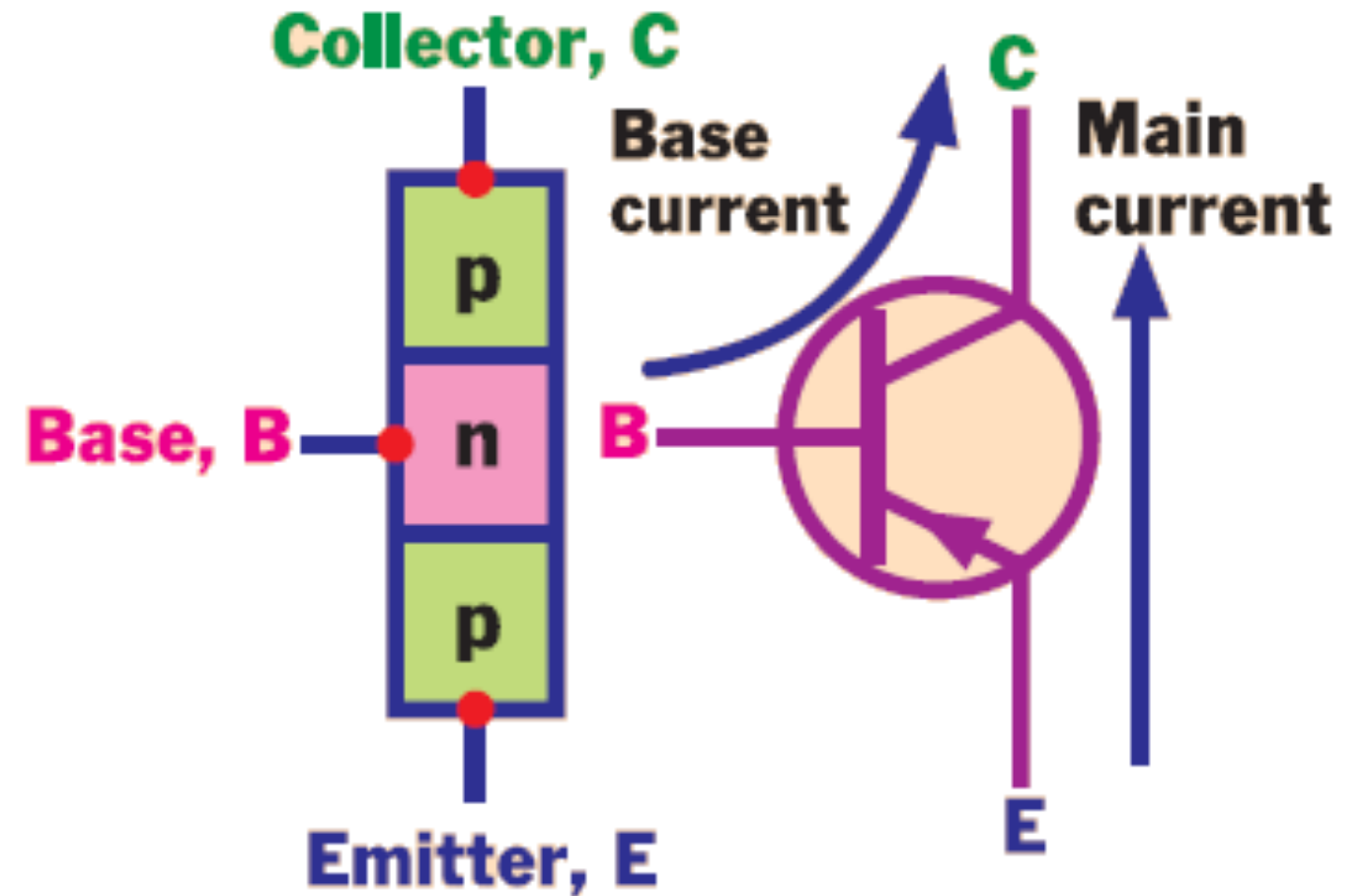

pnp transistor

Transistor as a current amplifier



Small $I_B \Rightarrow$ bigger I_C
When $I_B = 0, I_C = 0$

$$I_B \neq I_C$$


$$I_C > I_B$$

$$I_E > I_C > I_B$$


$$I_E = I_C + I_B$$

current
Amplification:

$$= \frac{\Delta I_C}{\Delta I_B}$$

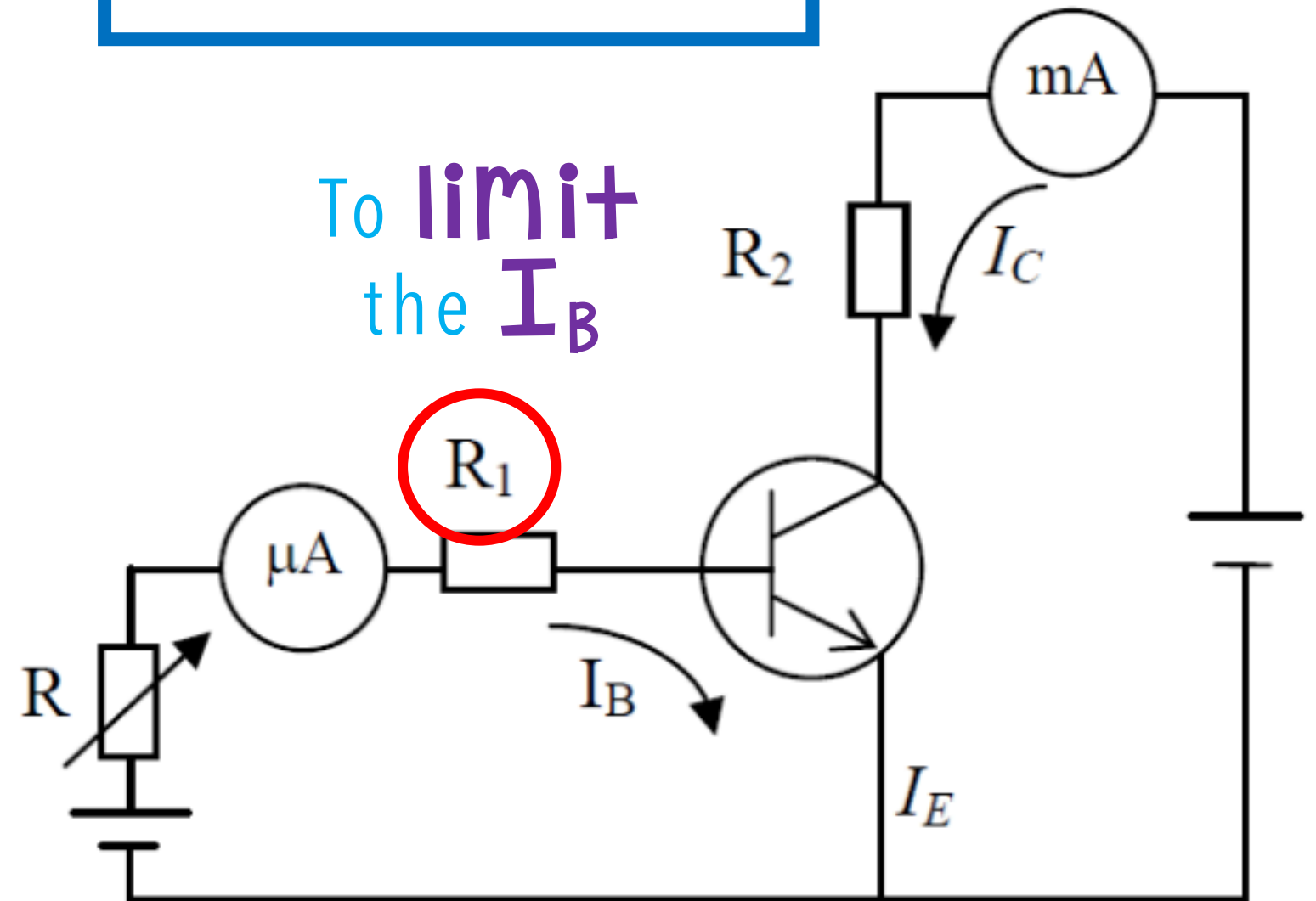

Transistor as a potential divider

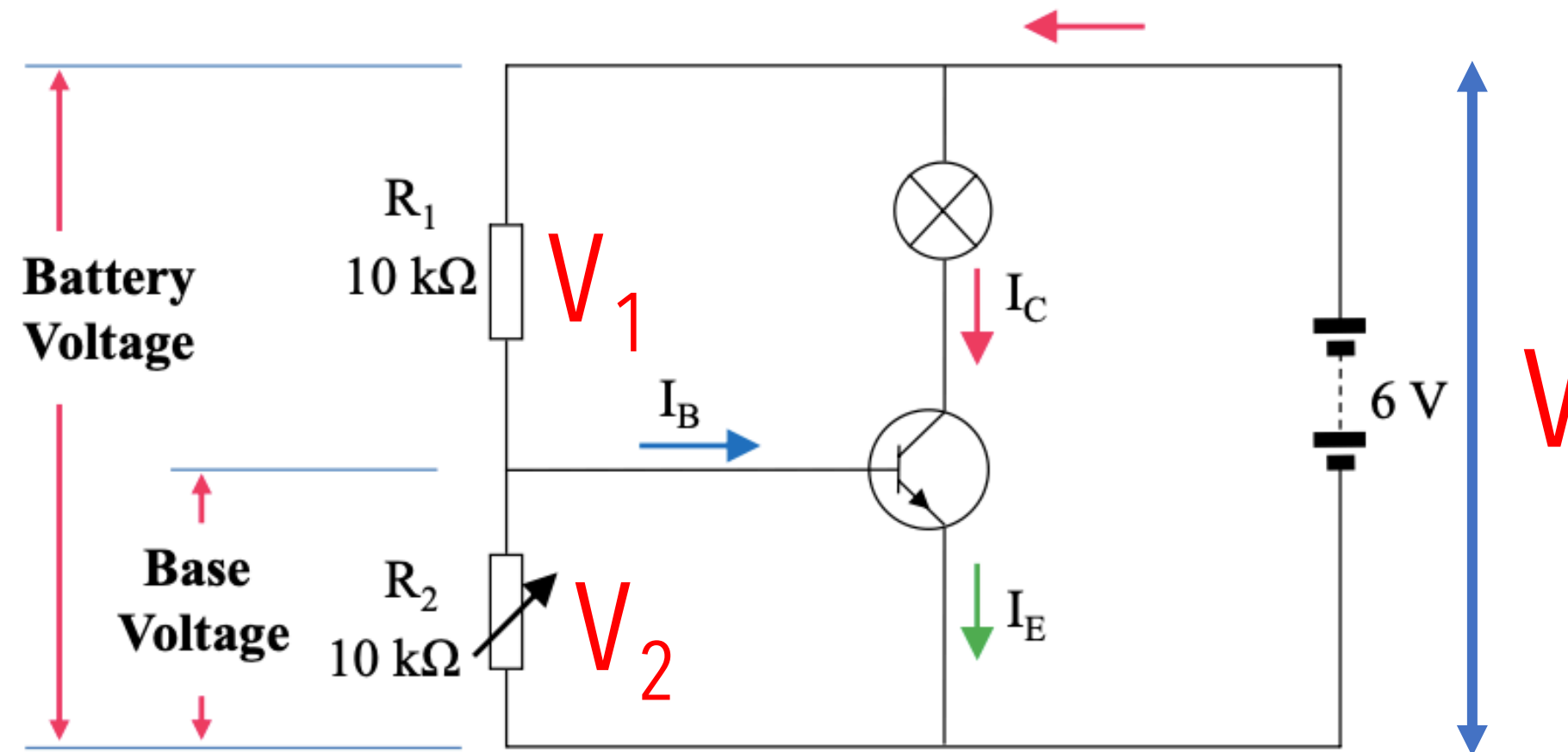

$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V \quad V_2 = \left(\frac{R_2}{R_1 + R_2} \right) V$$

$$V_1 + V_2 = V$$

The uses of transistor

LIGHT CONTROLLED SWITCH

1 Resistance of light-dependent resistor (LDR) rises considerably


2 Voltage across XY increases

3 Voltage across YZ decreases

4 Current I_B becomes very small and too low to switch the transistor on

6 Bulb does not light up

5 Current I_C becomes smaller

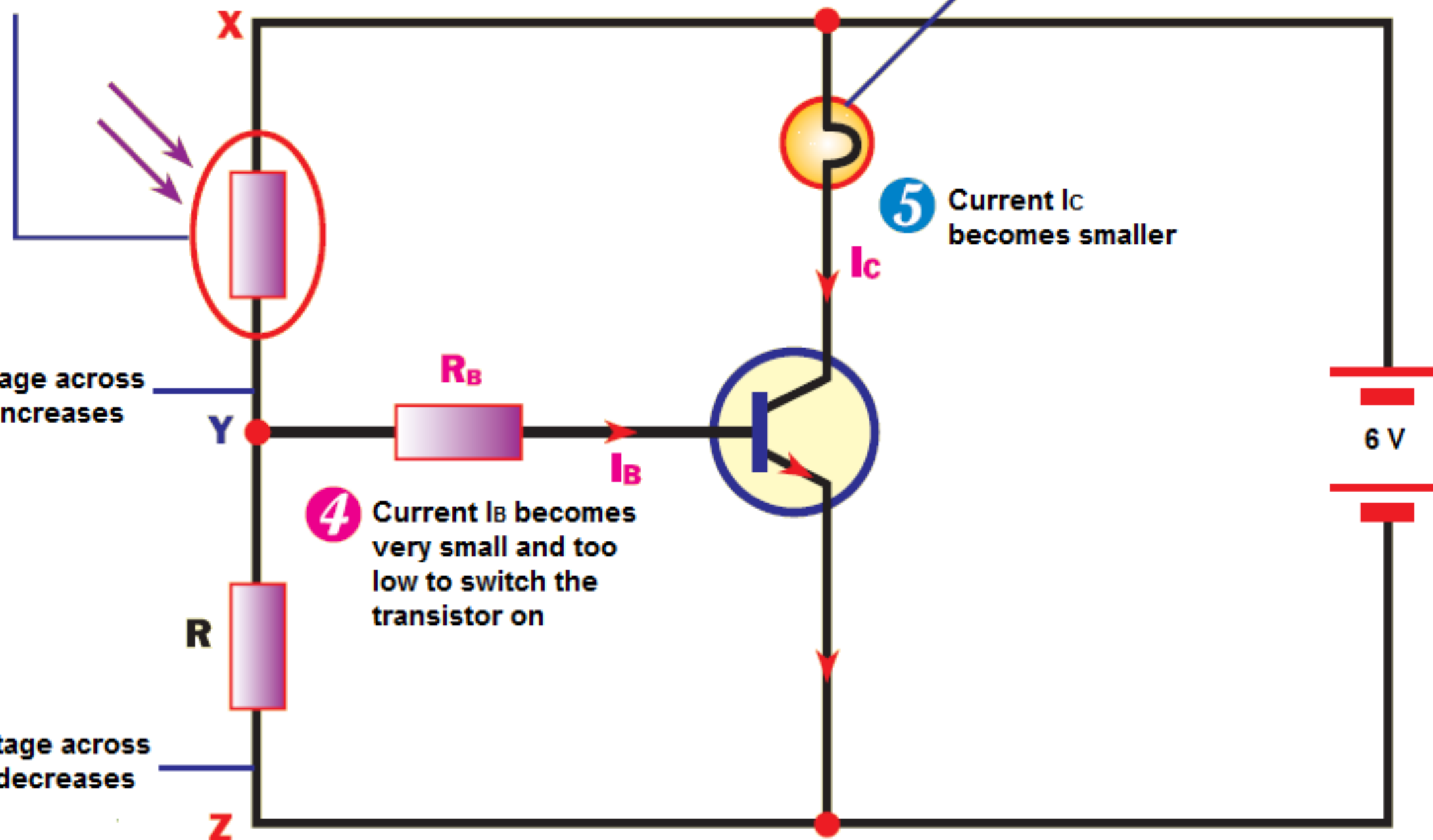




The uses of transistor

LIGHT CONTROLLED SWITCH

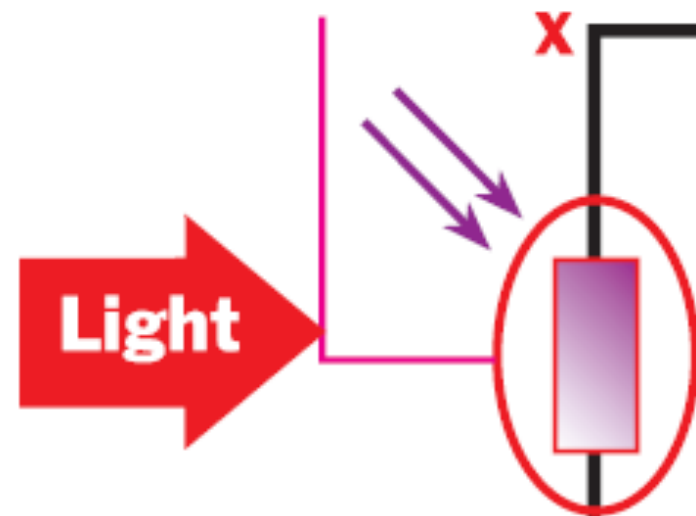1 Resistance of light-dependent resistor (LDR) decreases considerably




2 Voltage across XY decrease



3 Voltage across YZ increases

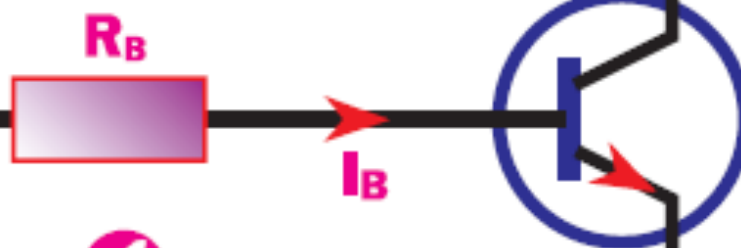4 Current I_B increases and high enough to switch the transistor on




5 Current I_C increases



6 Bulb lights up





HEAT CONTROLLED SWITCH

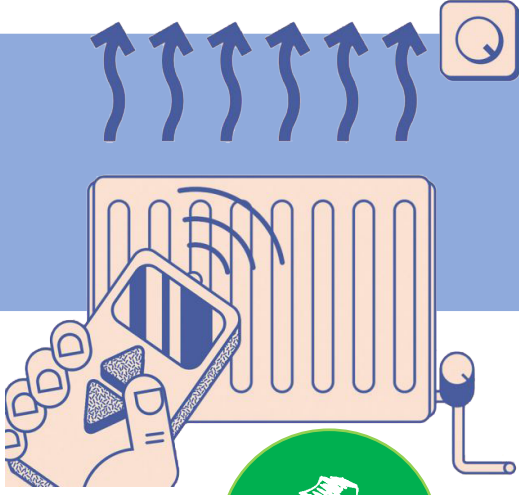

Temperature \uparrow
Resistance of
Thermistor \downarrow

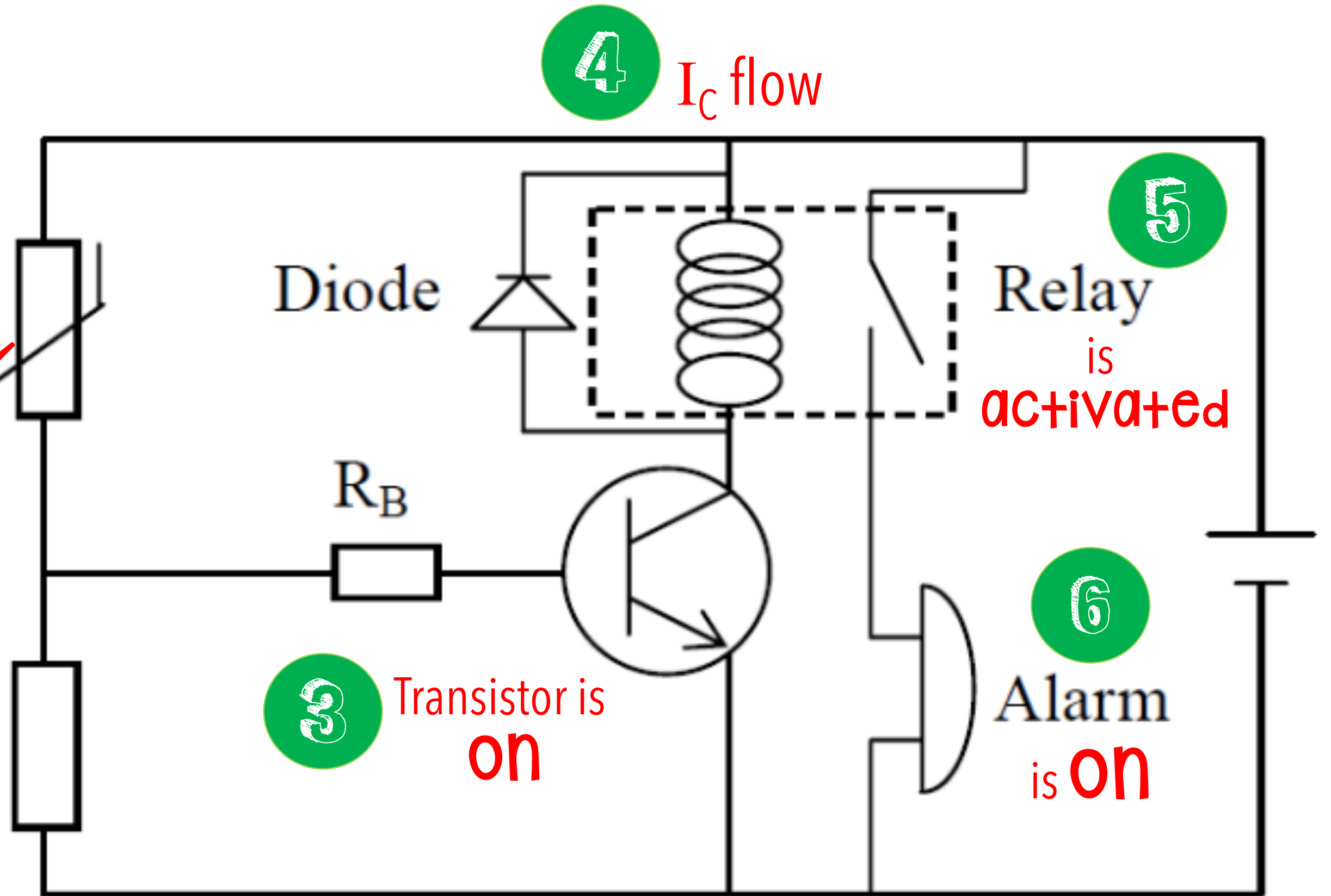$R \uparrow$ $V_B \uparrow$
 $\therefore I_B$ flow



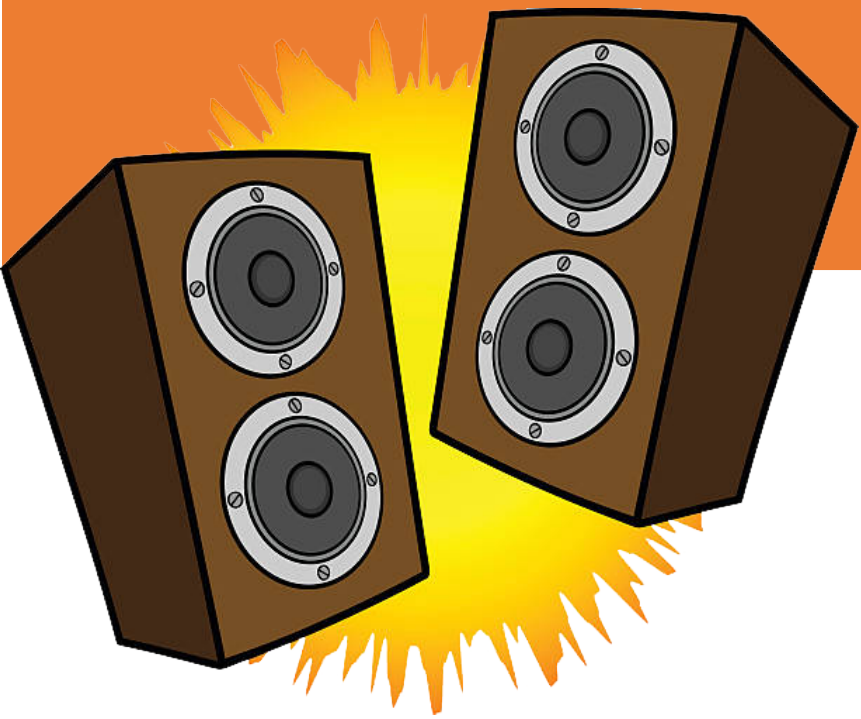

SOUND AMPLIFIER

5

Sound waves with higher amplitude is produced
Loud speaker

2


Capacitor allows the varying current flow it



Microphone

converts

audio (sound) signal → electrical

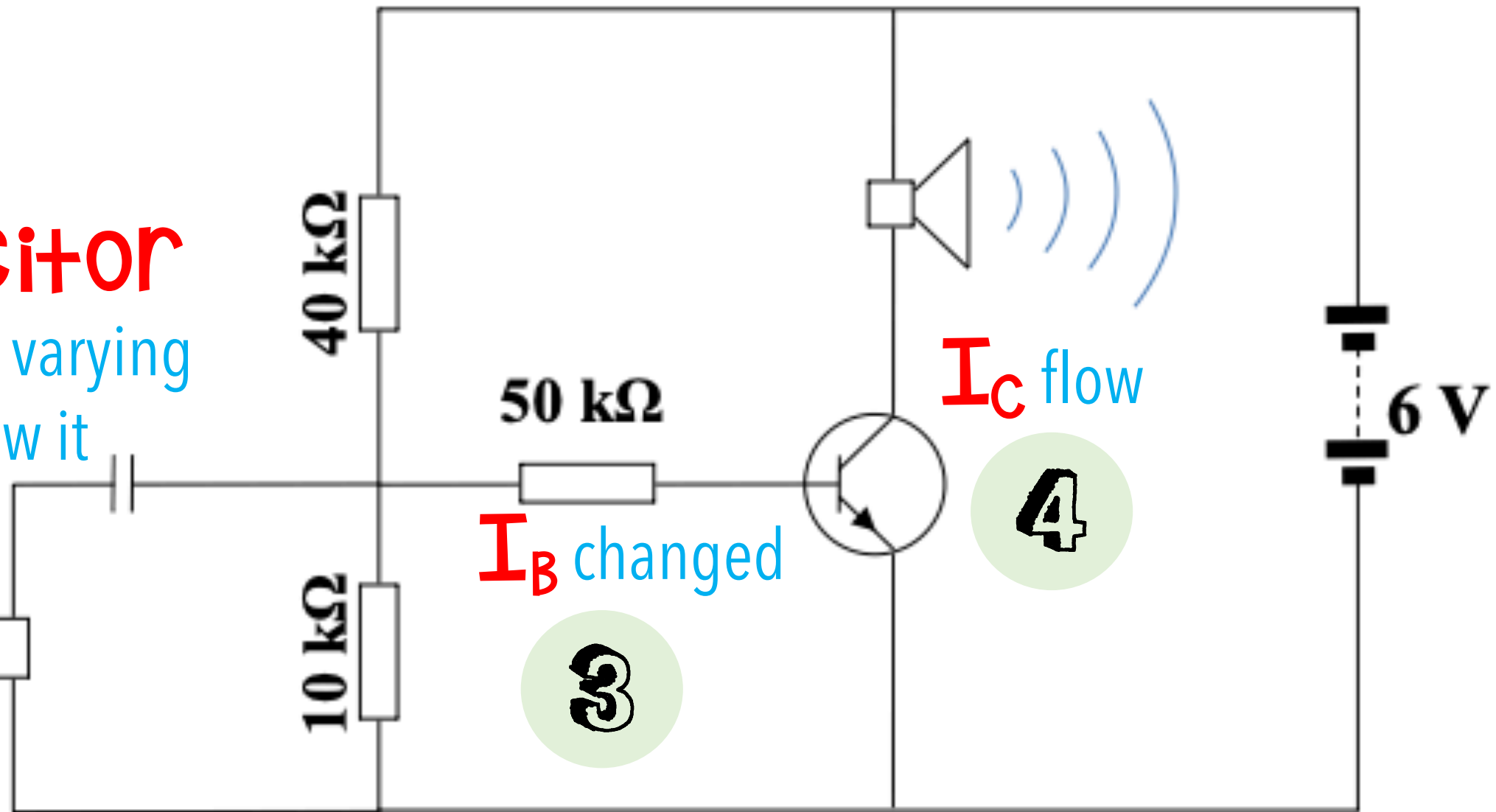

3

4

EXAMPLE:

Diagram 1 shows a simple cathode rays tube. Cathode emits electrons when switch P is closed.


(a) Name the process that enables the emission of electrons at the cathode.

Thermionic Emission

(b) State one reason why the extra high voltage is used

To accelerate the electron

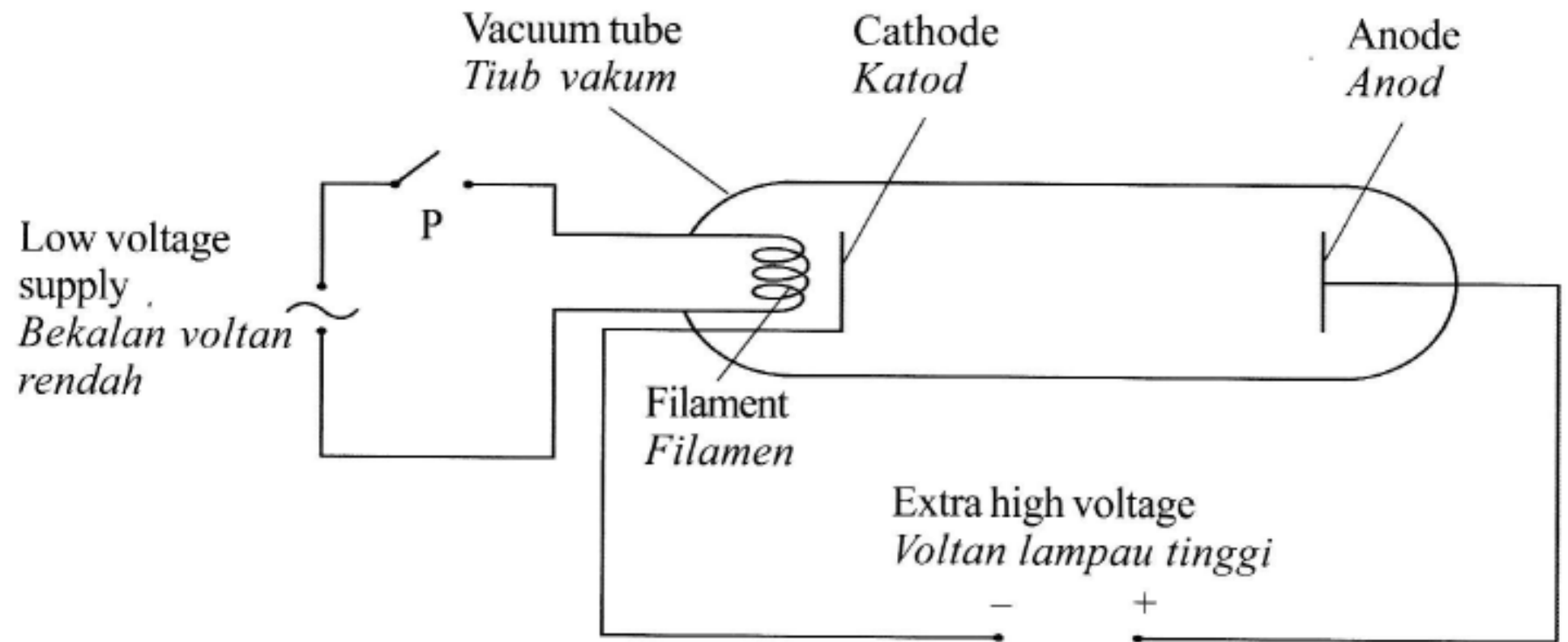
(c) complete the path of the cathode ray.



(d) When electrons flow in the cathode rays tube, the current produced in 5 seconds is 0.01A. Calculate the total charge of the electrons.

$$Q = I t = (0.01)(5)$$

$$Q = 0.05 \text{ C}$$

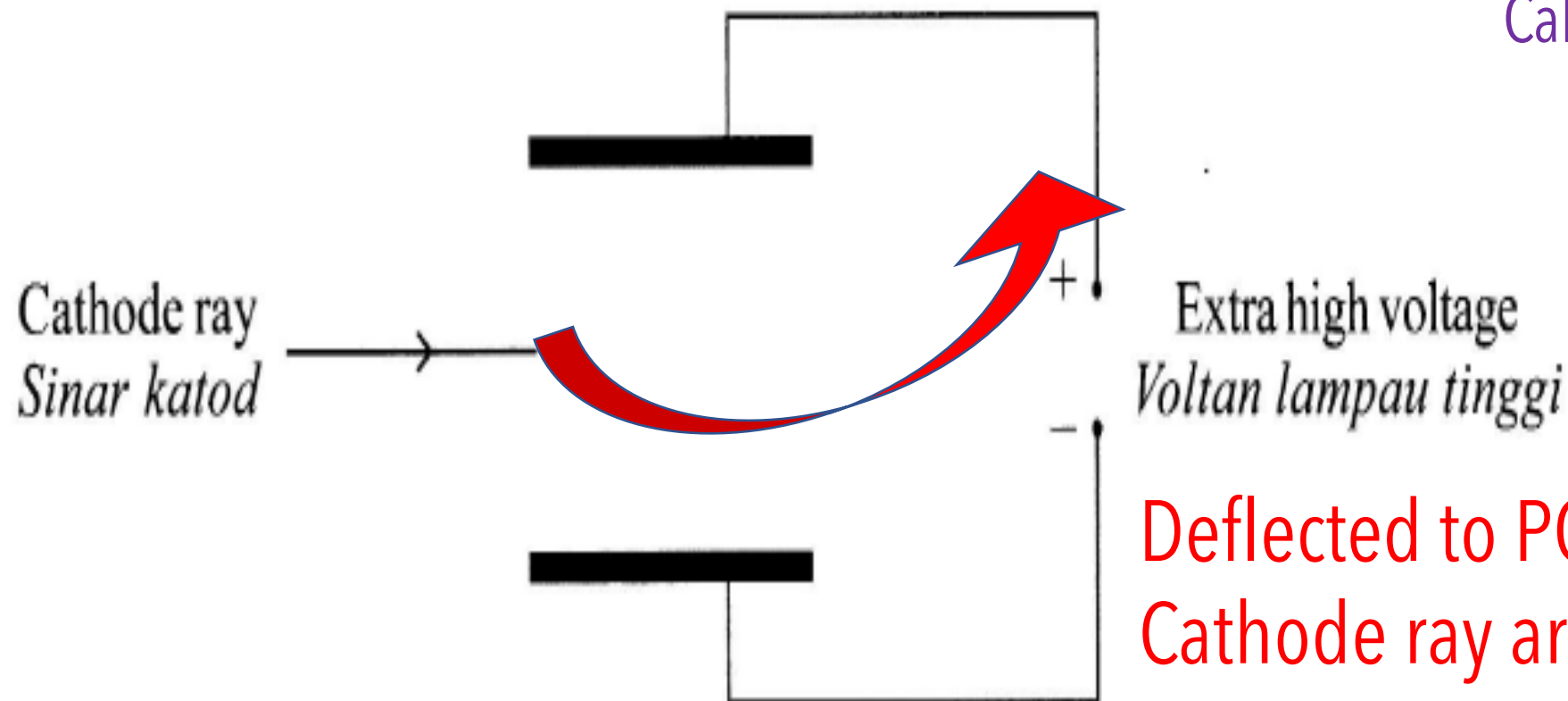

Deflected to POSITIVE
Cathode ray are negatively charge

EXAMPLE:

Diagram 2 shows a waveform on cathode ray oscilloscope (CRO) screen.
If the Y-input of CRO is set at 5.0 V cm^{-1} , what is the **peak voltage**?

Y-input : 5.0 V cm^{-1}


$$V_p = 2 \text{ div} \times \frac{5 \text{ V}}{\text{div}}$$

$$V_p = 10 \text{ V}$$

Extra: what is the **peak to peak voltage**?

$$V_{pp} = 4 \text{ div} \times \frac{5 \text{ V}}{\text{div}}$$

$$V_{pp} = 2 V_p = 20 \text{ V}$$

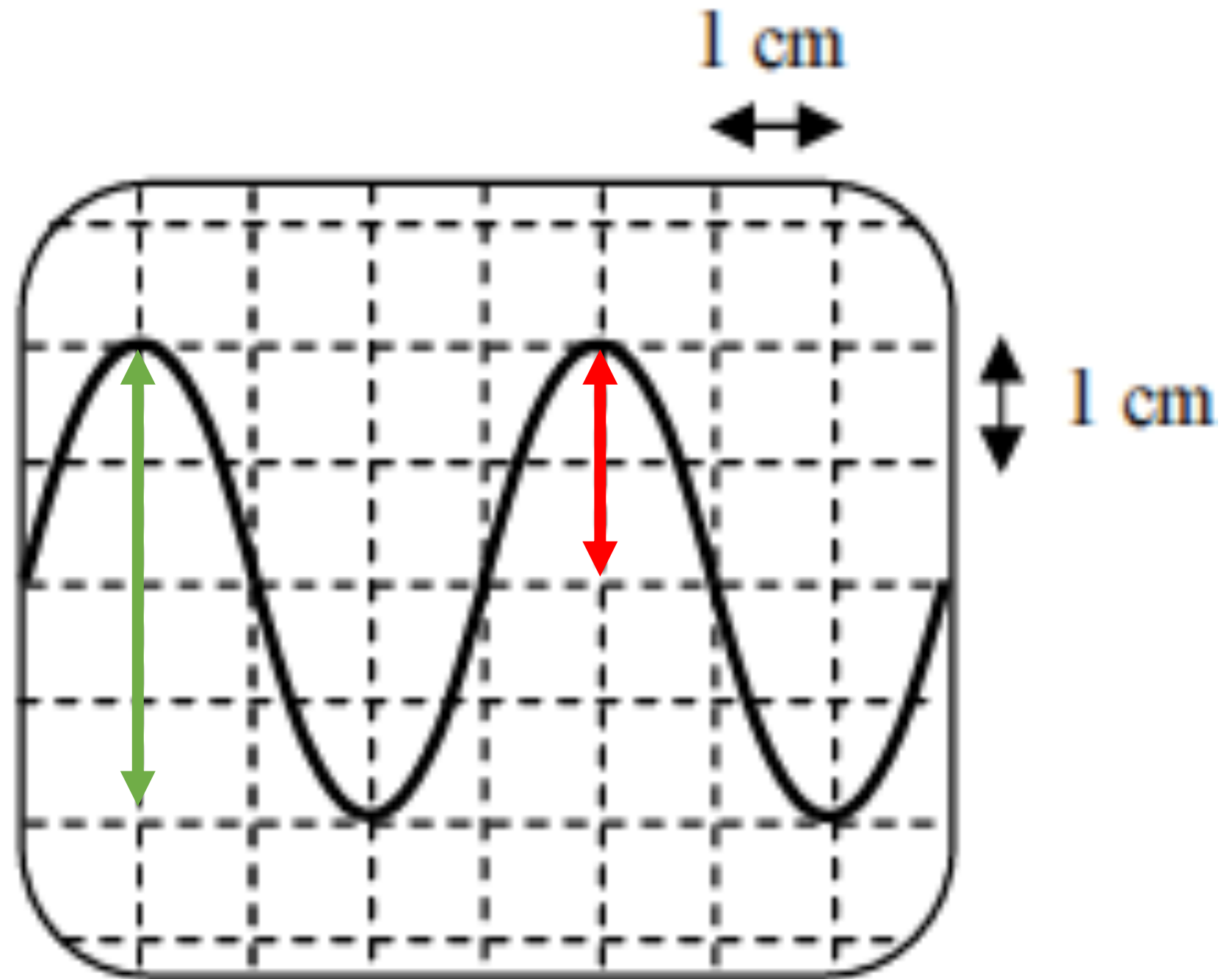

EXAMPLE:

Diagram 3 shows a circuit which acts as a switch to switch on an air conditioner, M, during the day only. P is a light dependent resistor which has a low resistance when its surroundings is bright.

Explain how the air conditioner, M, to be switched on.


- When LDR detect light, resistance of LDR ↓
- Resistance S ↑
- V_s ↑
 I_b flow to switch on the transistor
- I_c flow and relay is activated air conditioner, M is on

The air conditioner, M, with power rating 240 V, 2 kW, is switched on when V_s reaches 2.0 V. If the resistance of S is 10 kΩ, calculate the resistance of P.

$$V_s = \left(\frac{R_s}{R_p + R_s} \right) V$$

$$2 = \left(\frac{10k}{R_p + 10k} \right) 6$$

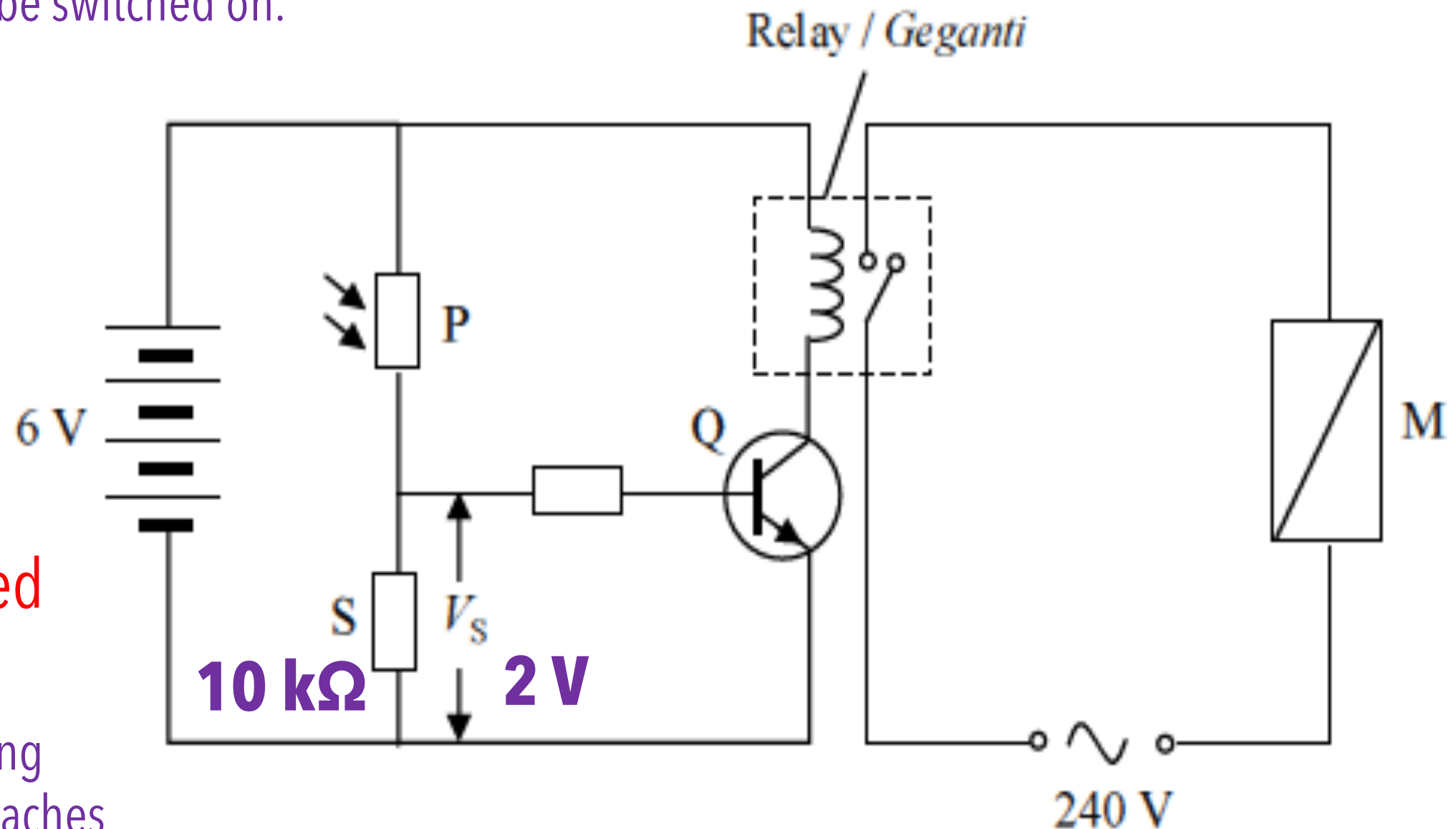$2R_p + 20k = 60k$
 $2R_p = 40k$
 $R_p = 20k\Omega$



Explain why the air conditioner is not connected directly to the transistor circuit.

Air conditioner needs higher voltage to activate which is 240 V

EXAMPLE:


Diagram 4 shows a circuit with a transistor that acts as an automatic switch. The resistance of resistor X is $40\text{ k}\Omega$ when it is in the **dark**. Calculate:

(a) The potential difference between T and U.

$$V_{TU} = \left(\frac{R_{TU}}{R_{ST} + R_{TU}} \right) V$$

$$V_{TU} = \left(\frac{40\text{ k}}{10\text{ k} + 40\text{ k}} \right) 6$$


$$V_{TU} = 4.8\text{ V}$$

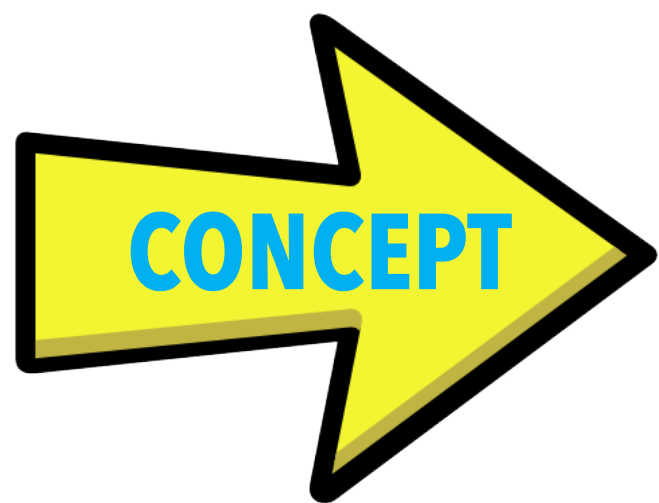

$$V_{ST} + V_{TU} = 6\text{ V}$$

$$V_{ST} + 4.8 = 6\text{ V}$$

$$V_{ST} = 1.2\text{ V}$$

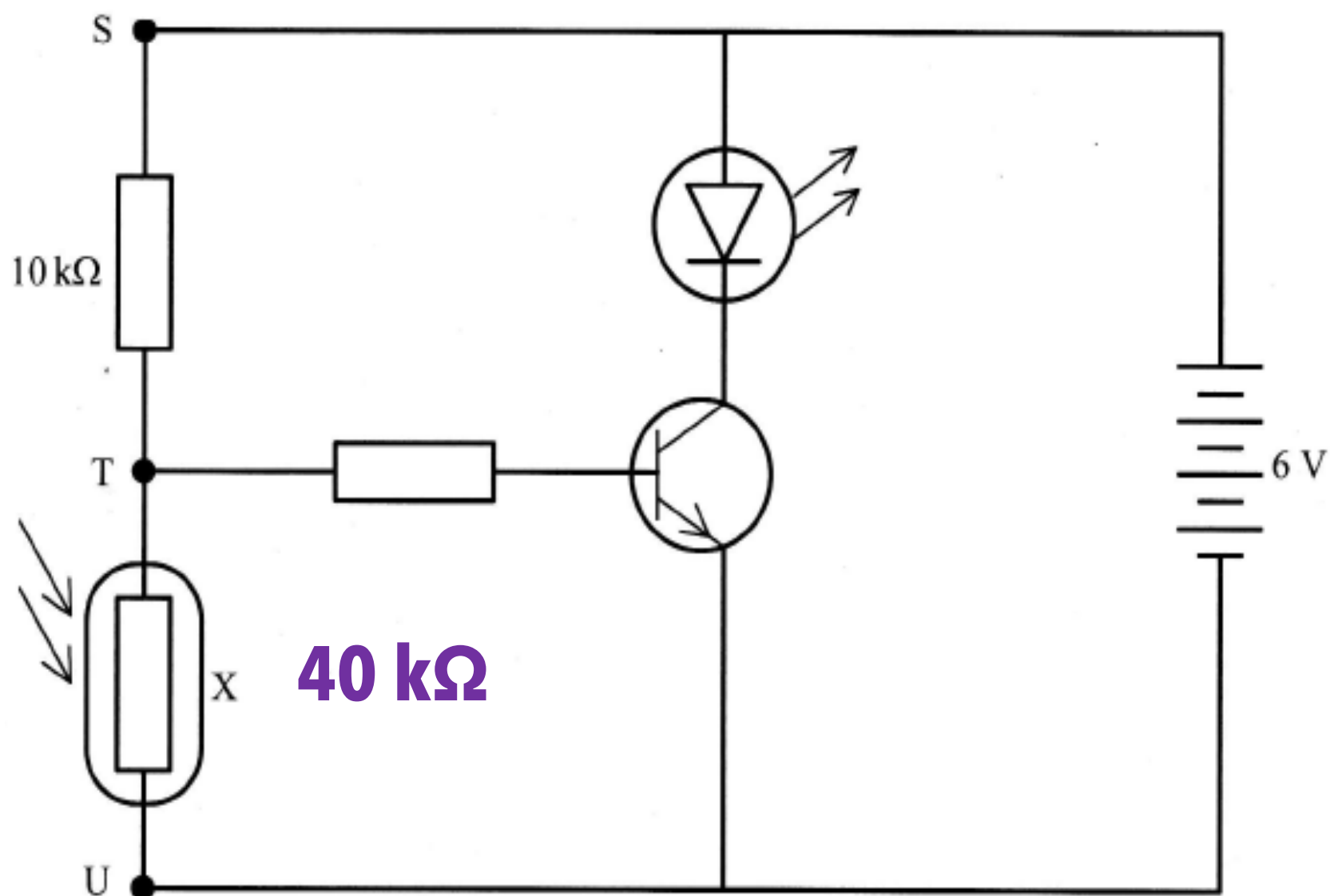

(b) The current flows through resistor X

$$V = IR$$

$$I = \frac{V}{R} = \frac{4.8}{40\text{ k}}$$

$$I = 1.2 \times 10^{-4}\text{ A}$$

Awesome
Physics
is around you

alinainarif

GREAT THINGS
NEVER
came from
**COMFORT
ZONES**





4.4

Logic Gate


has **one or more input** signals but only **one output** signal

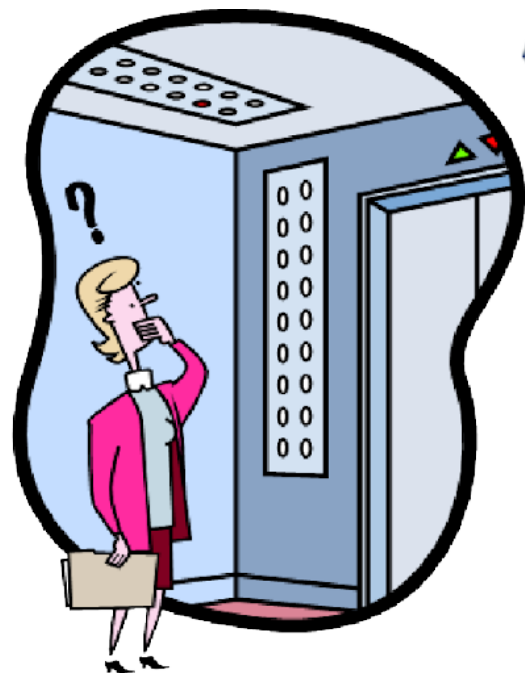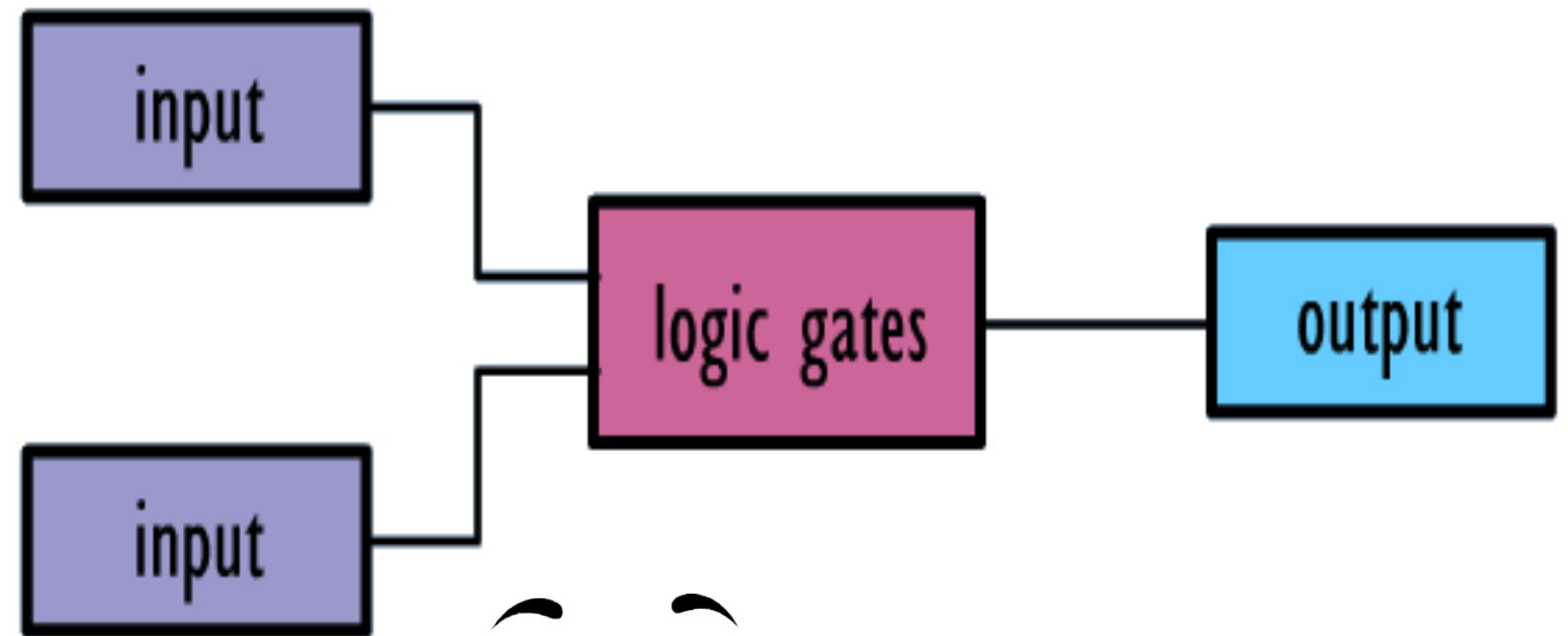1. Logic gates as **Switching Circuits** in electronic systems
2. Input and output signal of the logic gates can be either **high** (logic 1) or **low** (logic 0).





SYMBOL:

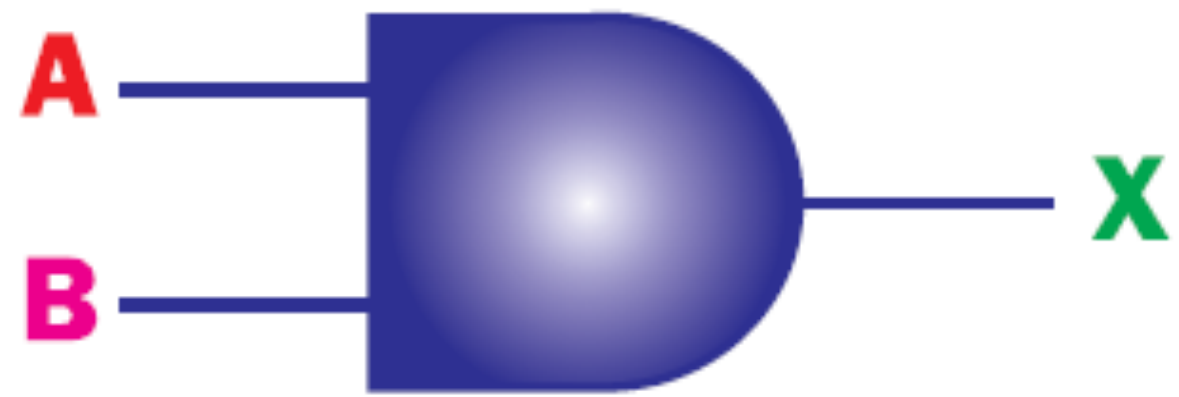


BOOLEAN EXPRESSION:

$$X = A \cdot B$$

TRUTH TABLE:

INPUT		OUTPUT
A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

CIRCUIT:

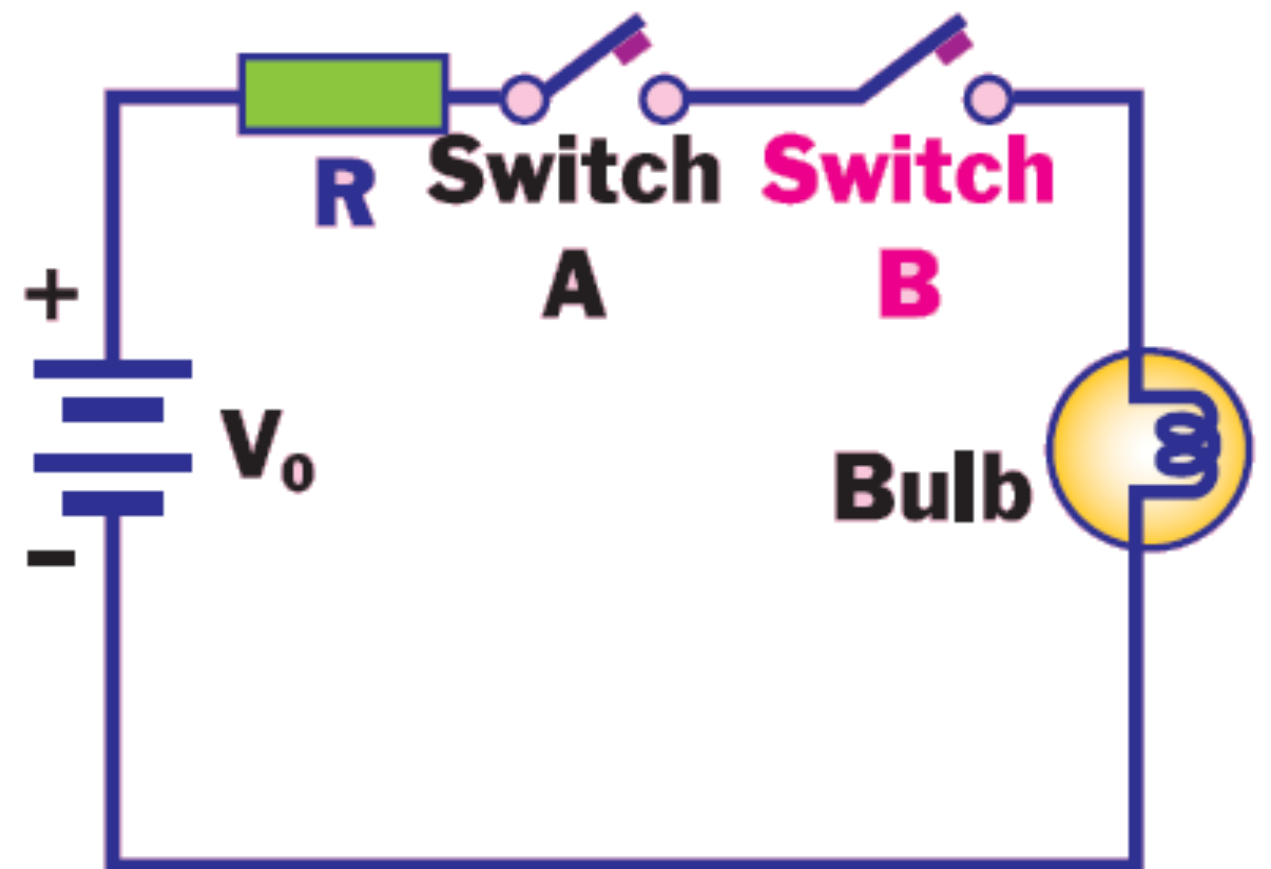



SYMBOL:




BOOLEAN EXPRESSION:

$$X = A + B$$

TRUTH TABLE:

INPUT		OUTPUT
A	B	X
0	0	0
0	1	1
1	0	1
1	1	1


CIRCUIT:

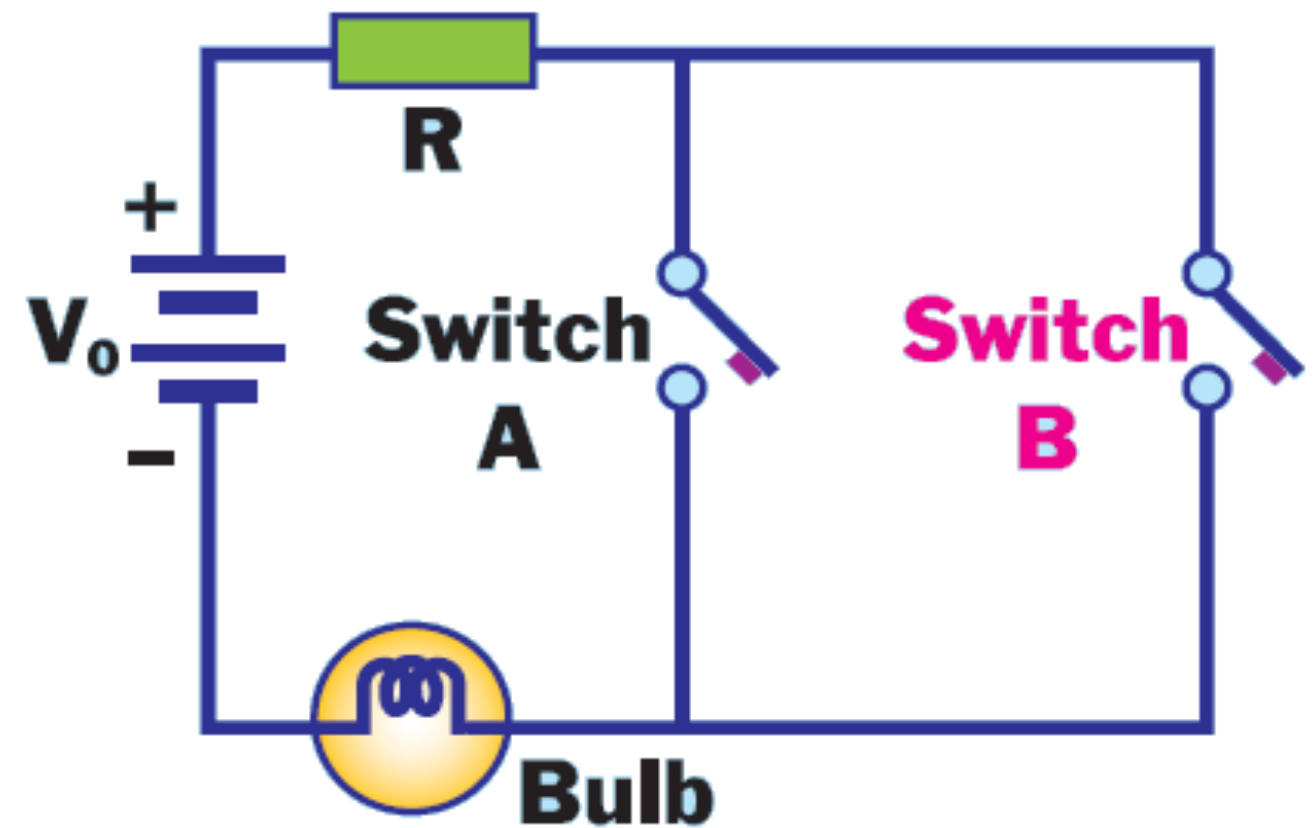



To **invert** the **input** signal

SYMBOL:

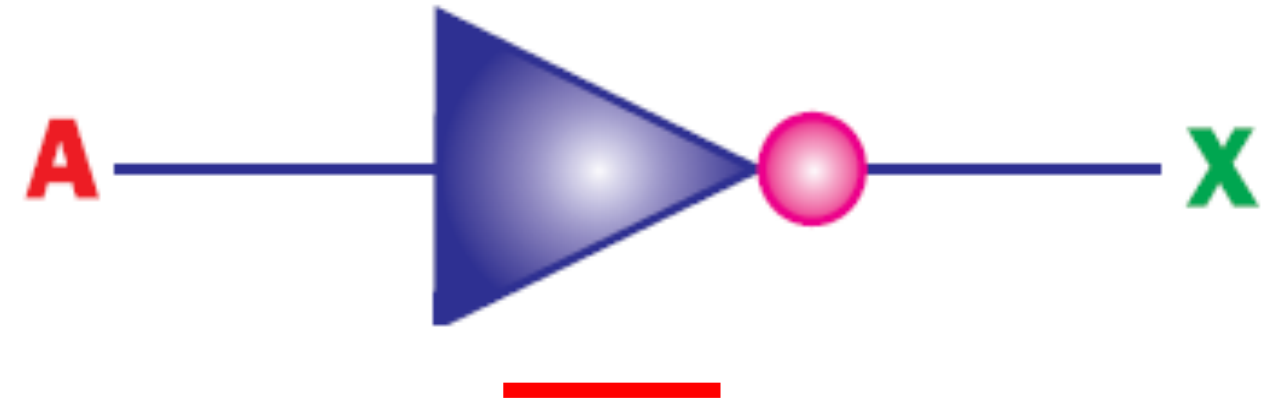


BOOLEAN EXPRESSION:


$$X = \overline{A}$$

TRUTH TABLE:

INPUT	OUTPUT
A	X
0	1
1	0

CIRCUIT:


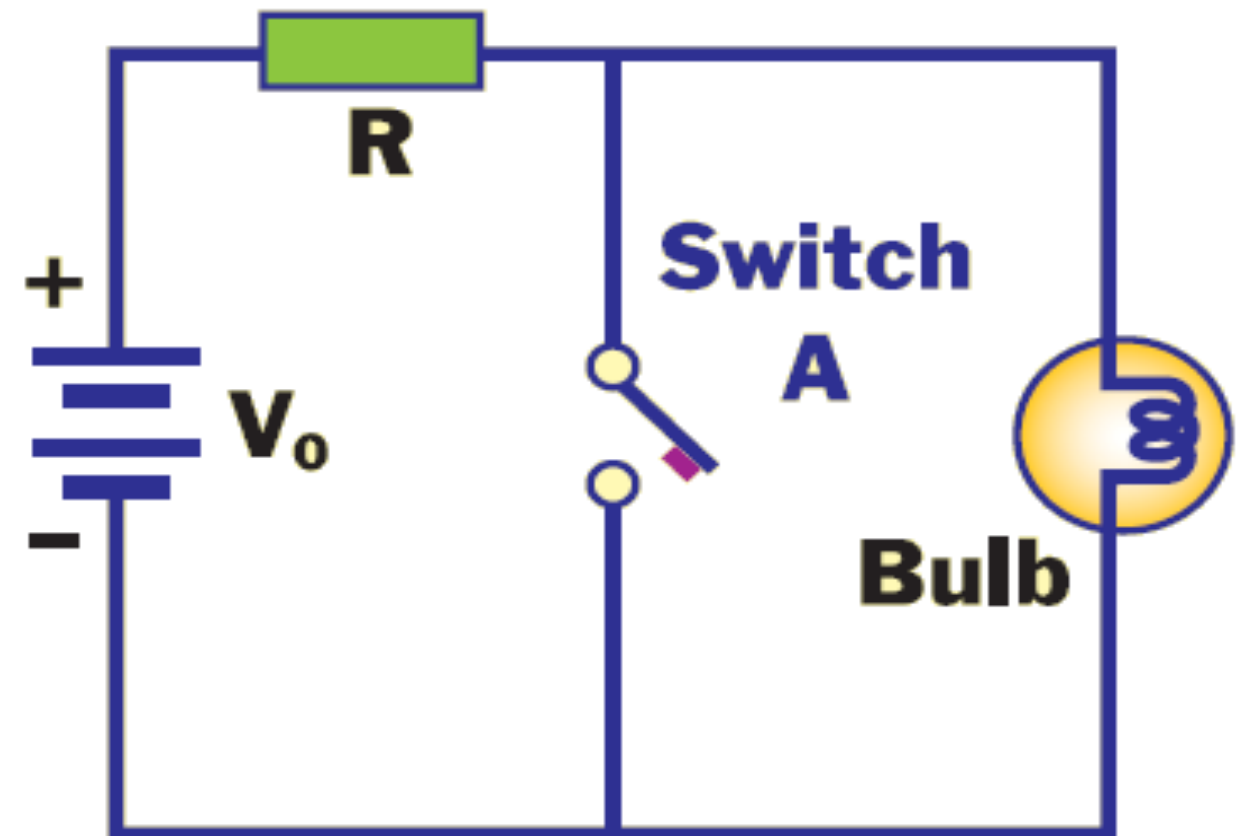


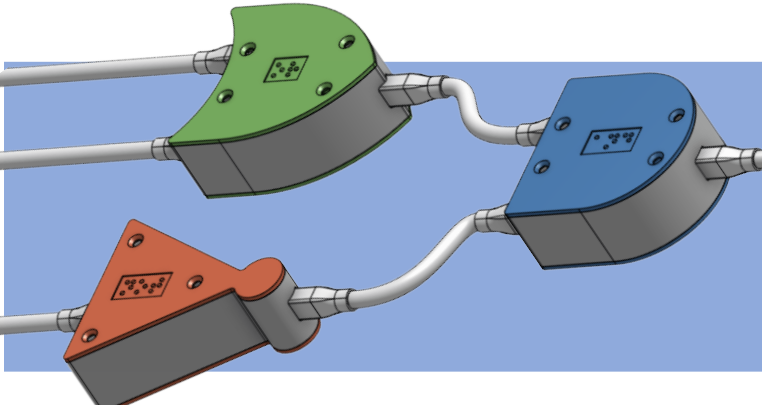

NAND Gate

NOR Gate

SYMBOL:

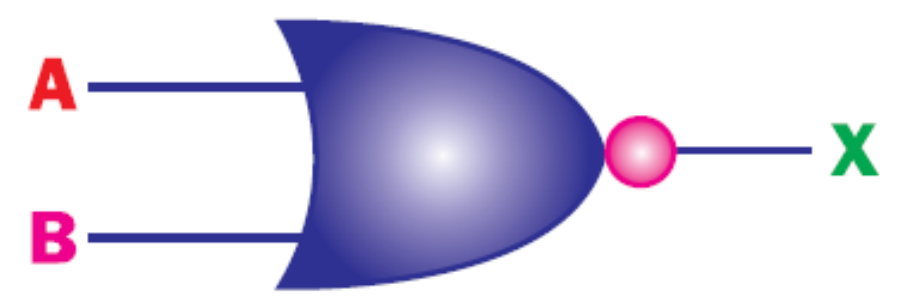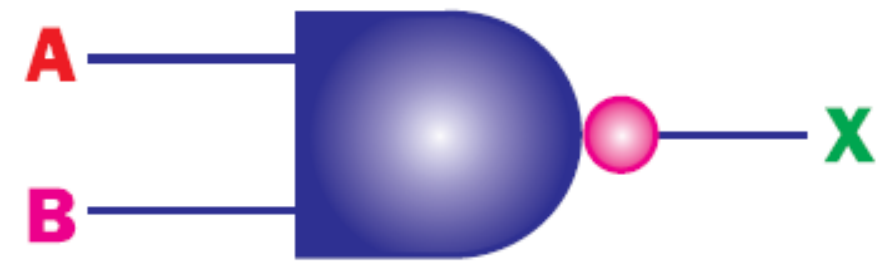

BOOLEAN
EXPRESSION:

$$X = \overline{A \cdot B}$$

$$X = \overline{A + B}$$


TRUTH TABLE:

INPUT		OUTPUT
A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

INPUT		OUTPUT
A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

COMBINATIONS OF LOGIC GATES

example

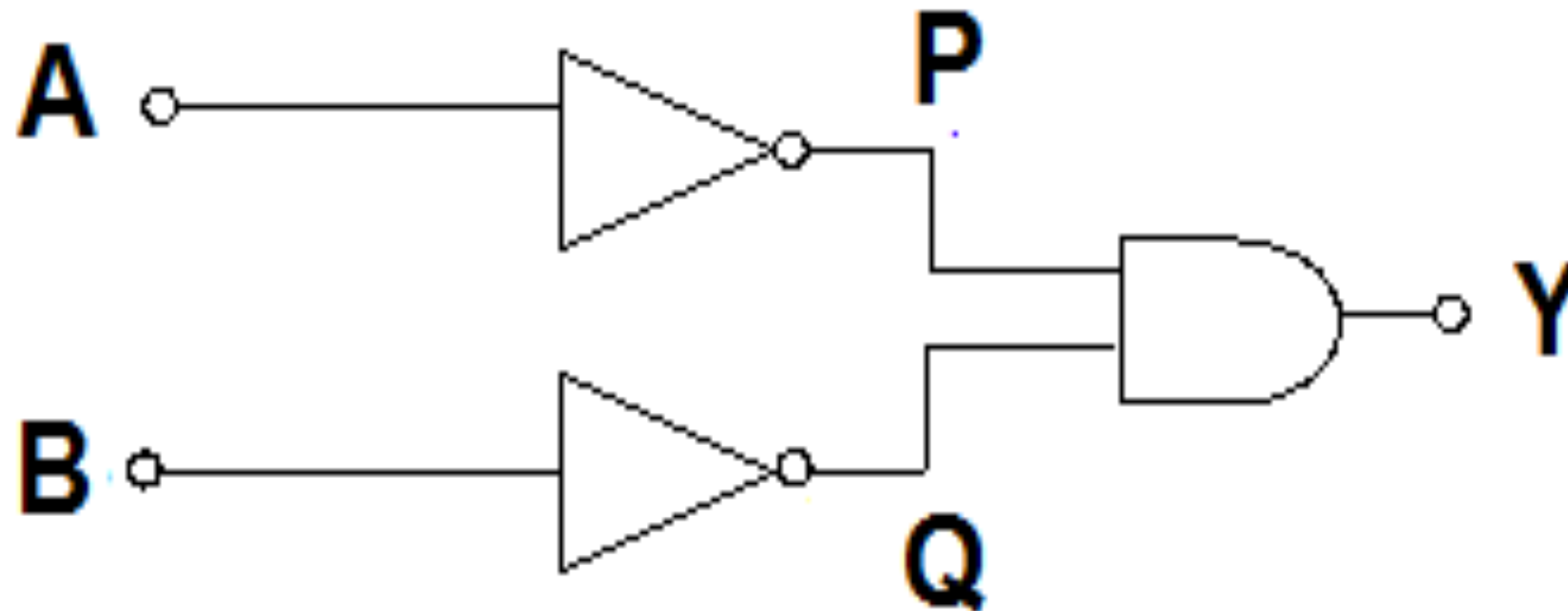


TRUTH TABLE:

INPUT		OUTPUT		
A	B	P	Q	Y
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

COMBINATIONS OF LOGIC GATES

example

2

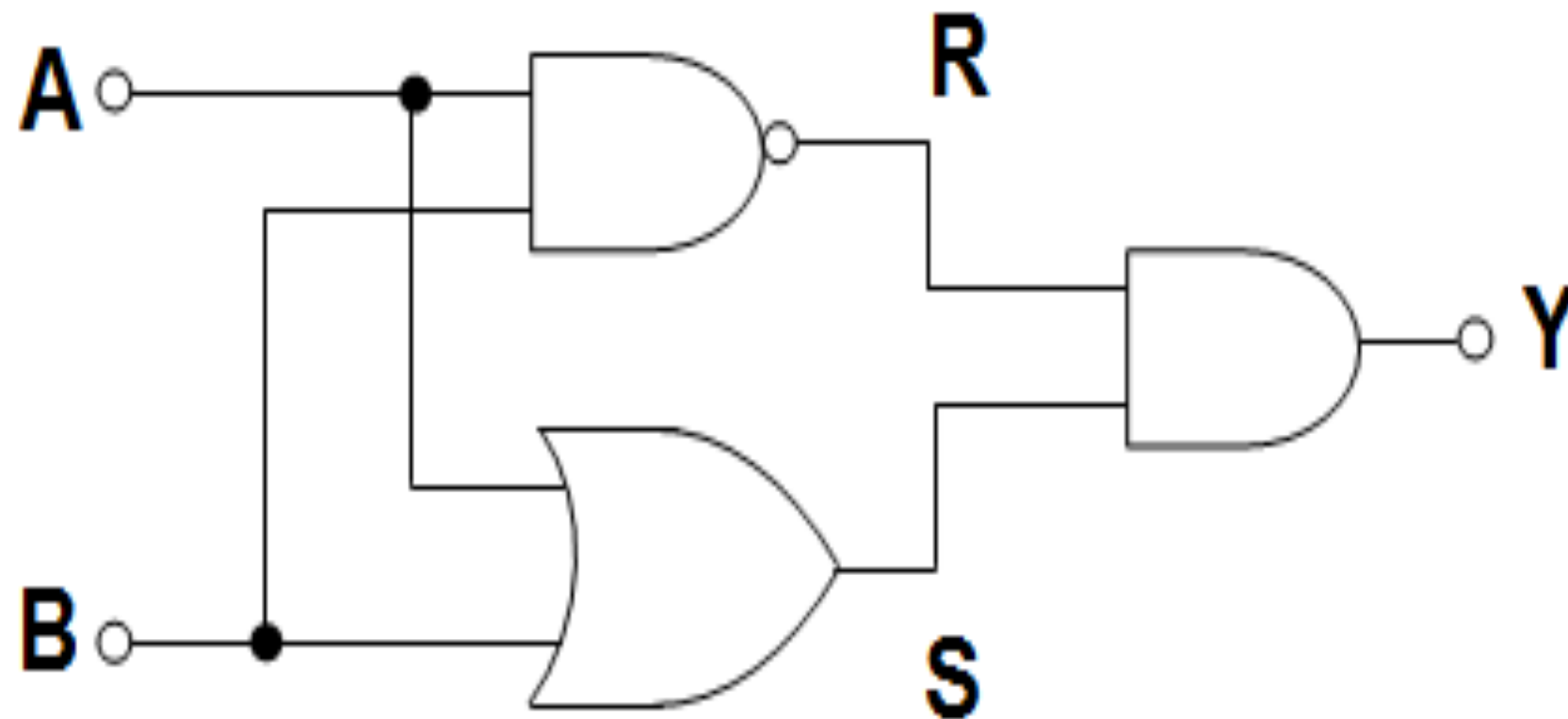

TRUTH TABLE:

INPUT		OUTPUT		
A	B	R	S	Y
0	0	1	0	0
0	1	1	1	1
1	0	1	1	1
1	1	0	1	0